

# Lecture 15

## Applications of feedback

- Oscillators
- Phase-locked loop

# Oscillators

feedback is widely used in *oscillators*, which generate sinusoidal signals to generate sinusoidal signal at frequency  $\omega_0$ ,


- closed-loop system should have poles at  $\pm j\omega_0$
- other poles should have negative real part (*i.e.*, other terms decay)

closed-loop pole at  $j\omega_0 \Leftrightarrow L(j\omega_0) = -1$ , *i.e.*,

$$\angle L(j\omega_0) = 180^\circ + q360^\circ, \quad |L(j\omega_0)| = 1$$

**intuition:** gain around whole loop, including  $-$  sign, is  $q360^\circ$ ; the feedback 'regenerates' the signal (at frequency  $\omega_0$ )

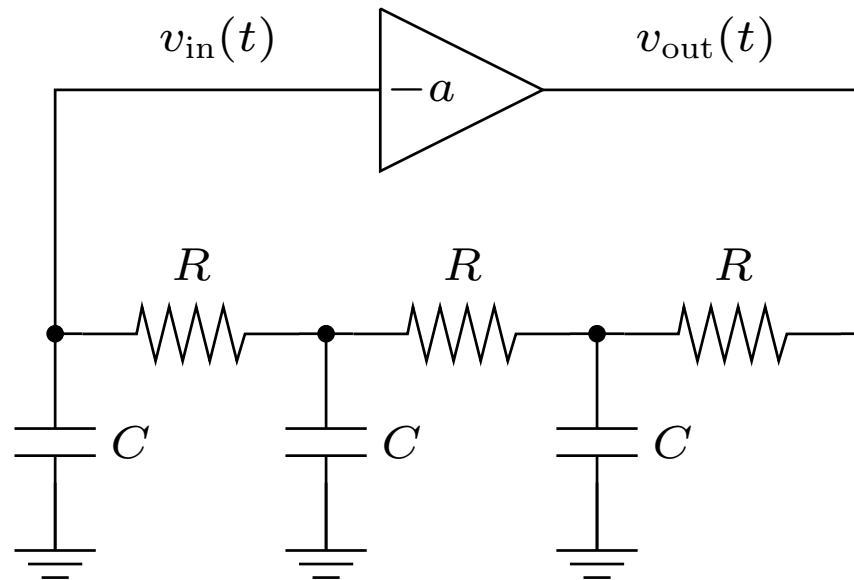**Example.** voltage amplifier has gain  $-a$ ,  $a > 0$




design variables:  $R$ ,  $C$ ,  $a$

transfer function of  $RC$  feedback network is

$$F(s) = \frac{V_{in}(s)}{V_{out}(s)} = \frac{1}{(sRC)^3 + 5(sRC)^2 + 6(sRC) + 1}$$

loop transfer function is  $L = aF$

Bode plot of  $F$ :

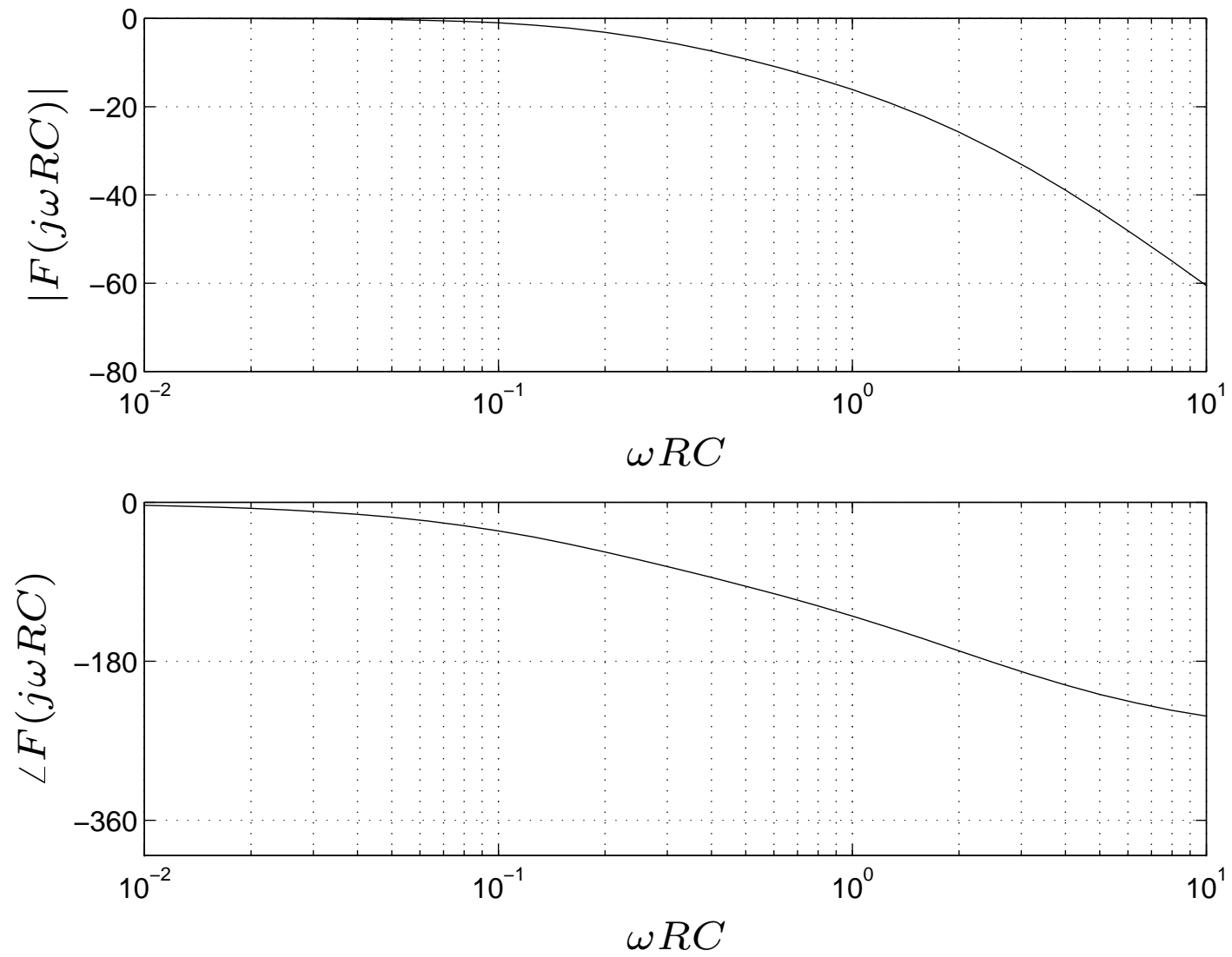

want loop transfer function  $L = aF = -1$  at  $\omega_0$

$$\angle L(j\omega_0) = \angle aF(j\omega_0) = \angle F(j\omega_0) = 180^\circ$$

from Bode phase plot we see  $\omega_0 \approx 2.5/(RC)$

from Bode magnitude plot we see  $F(\omega_0) \approx -30\text{dB}$ , so we need  $a \approx +30\text{dB}$

**analytically:**  $\angle L(j\omega_0) = 180^\circ$  is same as

$$\Im 1/L(j\omega_0) = \frac{1}{a} ((j\omega_0 RC)^3 + 6(j\omega_0 RC)) = 0$$

so  $\omega_0 = \sqrt{6}/(RC)$

hence  $L(j\omega_0) = \frac{a}{5(j\sqrt{6})^2 + 1} = -\frac{a}{29}$ , so we need  $a = 29$

**summary:** with gain  $a = 29$ , system oscillates at freq.  $\omega_0 = \sqrt{6}/(RC)$

(can check third pole is real & negative)

in practice, gain needs to be a little larger; nonlinearities limit amplitude of oscillation (careful analysis is hard)

intuitive analysis of  $RC$  oscillator:

- at  $\omega_0 = \sqrt{6}/(RC)$ ,  $RC$  network gives  $180^\circ$  loop phase shift
- amplifier gain  $a = 29$  makes up for amplitude loss of  $RC$  network at  $\omega_0$


# Phase-locked loop (PLL)

PLL is widely used to 'synchronize' one signal to another

applications:

- synchronize clocks, frequency multiplication/division
- video signal sync
- FM demodulation
- synchronize data communications transmitter, receiver
- track varying frequency source (*e.g.*, Doppler from space vehicle or aircraft)

basic PLL block diagram:

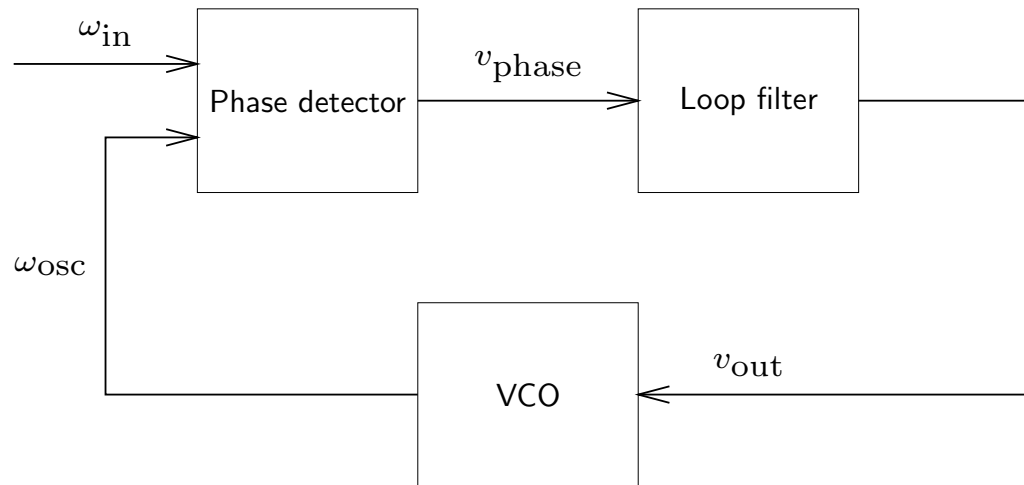

- signals on left (marked  $\omega_{in}$ ,  $\omega_{osc}$ ) are frequency-varying sinusoids, of form  $\cos(\omega(t)t)$ ; *instantaneous frequency*  $\omega(t)$  varies only a small amount around some fixed value
- signals on right ( $v_{phase}$ ,  $v_{out}$ ) are (usually) voltages

**idea:** feedback from phase detector adjusts voltage controlled oscillator (VCO) frequency to match input frequency



# Phase detector

phase detector generates voltage proportional to phase difference of frequency-varying sinusoids

$$v_{\text{phase}}(t) = k_{\text{det}} \theta_{\text{err}}(t)$$
$$\theta_{\text{err}}(t) = \int_0^t (\omega_{\text{in}}(\tau) - \omega_{\text{osc}}(\tau)) d\tau$$

**provided** phase difference  $\theta_{\text{err}}$  is less than  $\pm 90^\circ$  or so

$k_{\text{det}}$  is the detector gain (V/rad)

# Voltage controlled oscillator

VCO generates frequency-varying sinusoid, with frequency depending on its input voltage  $v_{\text{out}}(t)$ :


$$\omega_{\text{osc}}(t) = \omega_{\text{free}} + k_{\text{osc}}v_{\text{out}}(t)$$

- $\omega_{\text{free}}$  is called the *free running frequency*
- $k_{\text{osc}}$  is the VCO gain (in (rad/sec)/V)

real VCOs have a minimum and maximum frequency
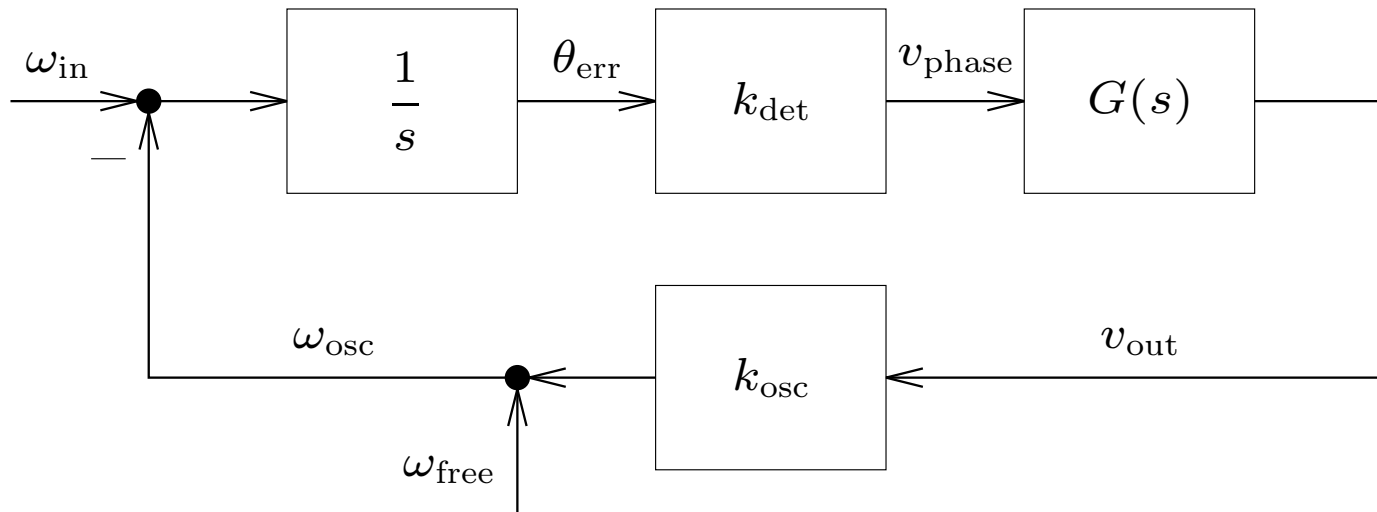
# LTI analysis of PLL

loop filter is often LTI, *i.e.*, T.F.  $G(s)$



this LTI model of PLL is good **provided**

- $|\theta_{err}| \leq 90^\circ$  (or so)
- $\omega_{osc}$  stays within limits

transfer function from  $\omega_{\text{free}}$  to  $\omega_{\text{osc}}$  is

$$\frac{s}{s + k_{\text{det}}k_{\text{osc}}G(s)}$$

which is zero at  $s = 0$ , so  $\omega_{\text{free}}$  does not affect  $\omega_{\text{osc}}$  (in steady-state)

transfer function  $H$  from  $\omega_{\text{in}}$  to  $\omega_{\text{osc}}$  is

$$H(s) = \frac{k_{\text{det}}k_{\text{osc}}G(s)/s}{1 + k_{\text{det}}k_{\text{osc}}G(s)/s} = \frac{k_{\text{det}}k_{\text{osc}}G(s)}{s + k_{\text{det}}k_{\text{osc}}G(s)}$$

phase detector gives integral action:  $H(0) = 1$

for constant  $\omega_{\text{in}}$ ,  $\omega_{\text{osc}}(t) \rightarrow \omega_{\text{in}}$  as  $t \rightarrow \infty$ ,  
*i.e.*, VCO frequency locks to input frequency

# First order loop

simplest PLL uses  $G(s) = 1$ , which yields

$$H(s) = \frac{1}{1 + s/(k_{\text{det}}k_{\text{osc}})}$$

(hence the name 'first order')

- $k_{\text{osc}}k_{\text{det}}$  is called *loop bandwidth*
- $\omega_{\text{osc}}(t)$  tracks  $\omega_{\text{in}}(t)$ , with time constant  $1/(k_{\text{det}}k_{\text{osc}})$

## Second order loop

very common PLL uses lowpass loop filter

$$G(s) = \frac{1}{1 + s/\omega_{\text{loop}}}$$

which yields

$$H(s) = \frac{1}{1 + s/(k_{\text{det}}k_{\text{osc}}) + s^2/(\omega_{\text{loop}}k_{\text{det}}k_{\text{osc}})}$$

(hence the name 'second order')


common choices for  $\omega_{\text{loop}}$ :

- $\omega_{\text{loop}} = 4k_{\text{det}}k_{\text{osc}}$  (sets both poles of  $H$  to  $-\omega_{\text{loop}}/2 = -2k_{\text{det}}k_{\text{osc}}$ )
- $\omega_{\text{loop}} = 2k_{\text{det}}k_{\text{osc}}$   
(sets poles of  $H$  to  $(-1 \pm j)\omega_{\text{loop}}/2 = (-1 \pm j)k_{\text{det}}k_{\text{osc}}$ )


$\omega_{\text{osc}}$  is 2nd order lowpass filtered version of  $\omega_{\text{in}}$

# Phase detectors

basic idea of common phase detector:

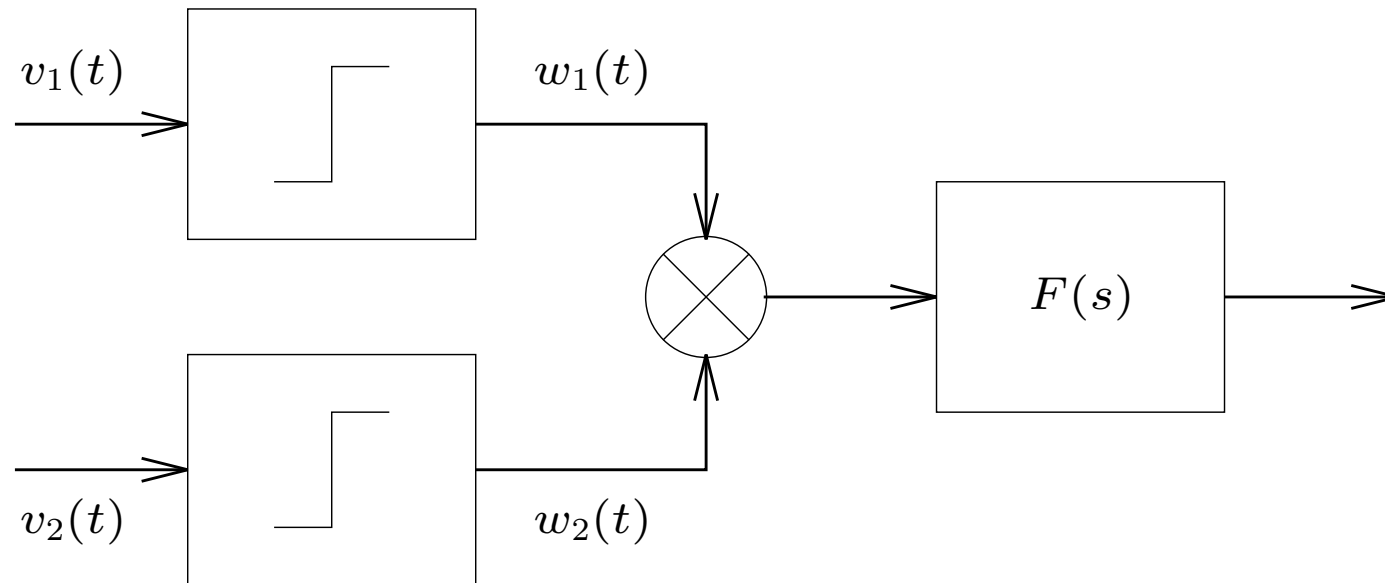


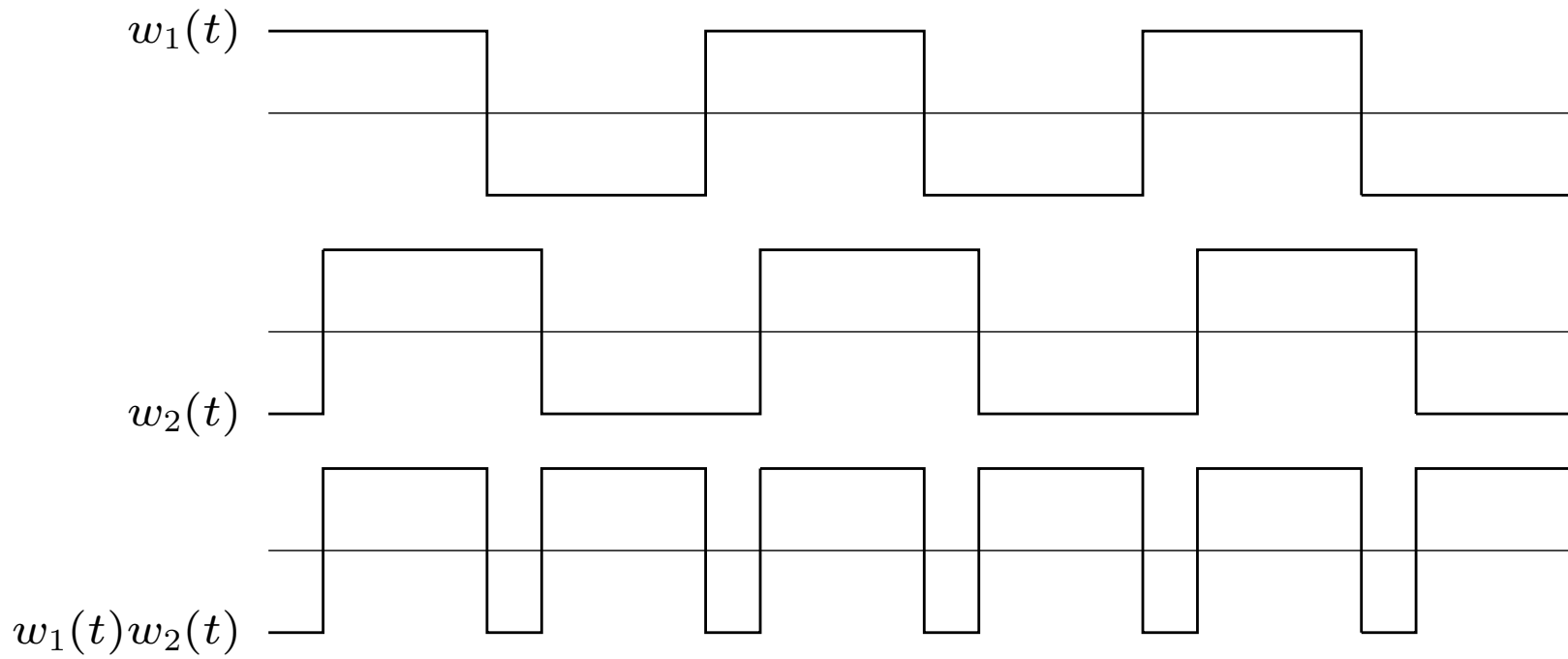- input signals are converted to squarewaves, then multiplied
- lowpass filtered (averaged) by  $F(s)$





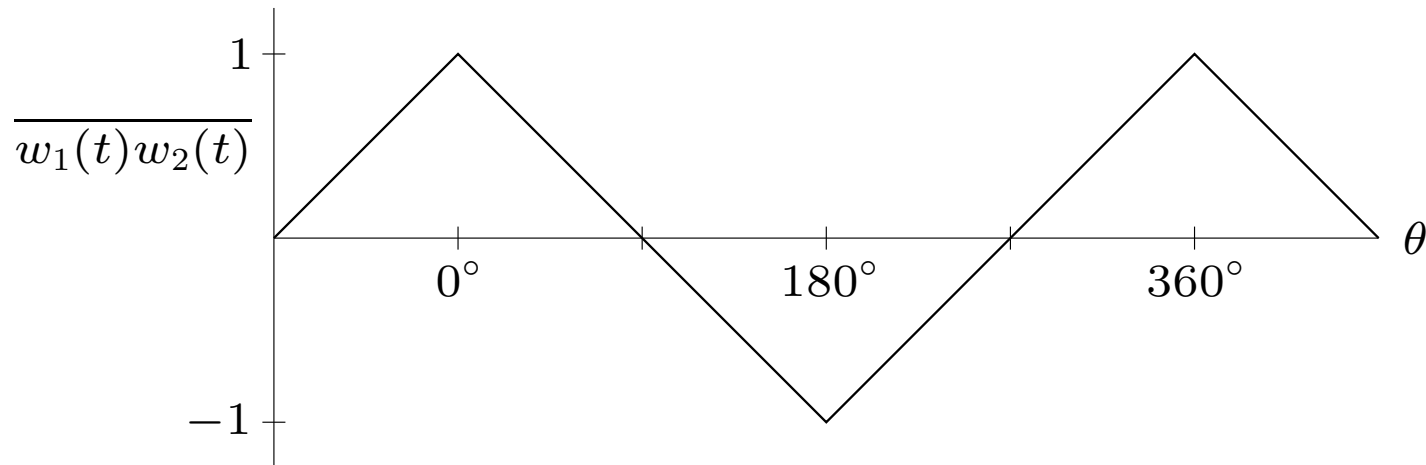average value of  $w_1(t)w_2(t)$  depends on phase difference  $\theta$ :



- this phase detector operates between  $0^\circ$  and  $180^\circ$  instead of  $\pm 90^\circ$ ; doesn't affect PLL
- if bandwidth of lowpass filter is  $\ll$  input frequencies, its output  $\approx \overline{w_1(t)w_2(t)}$
- phase detector is linear (plus constant) for  $0 \leq \theta \leq 180^\circ$

## Lock range

**lock range:** range of  $\omega_{\text{in}}$  over which can the PLL can maintain 'lock'

recall that we must have  $|\theta_{\text{err}}| < \pi/2$  or so for linear phase detector operation

transfer function from  $\omega_{\text{in}} - \omega_{\text{free}}$  to  $\theta_{\text{err}}$ :

$$F(s) = \frac{1}{s + k_{\text{det}}k_{\text{osc}}G(s)}$$

for  $\omega_{\text{in}}$  constant, we have in steady-state

$$\theta_{\text{err}} = F(0)(\omega_{\text{in}} - \omega_{\text{free}}) = \frac{\omega_{\text{in}} - \omega_{\text{free}}}{k_{\text{det}}k_{\text{osc}}G(0)}$$

so lock range for slowly varying  $\omega_{\text{in}}$  is

$$|\omega_{\text{in}} - \omega_{\text{free}}| \leq (\pi/2)k_{\text{det}}k_{\text{osc}}G(0)$$

lock range analysis for rapidly varying  $\omega_{\text{in}}$ :

assume  $|\omega_{\text{in}}(t) - \omega_{\text{free}}(t)| \leq \Omega$  for all  $t$

$$\theta_{\text{err}} = f * (\omega_{\text{in}} - \omega_{\text{free}})$$

where  $f$  is impulse response of  $F$

by peak-gain analysis, peak of  $\theta_{\text{err}}(t)$  is no more than

$$\Omega \int_0^{\infty} |f(\tau)| d\tau$$

so lock occurs for

$$\Omega \int_0^{\infty} |f(\tau)| d\tau \leq \pi/2$$

**first order loop filter** ( $G(s) = 1$ ):

$$F(s) = \frac{1}{s + k_{\text{det}}k_{\text{osc}}}, \quad f(t) = e^{-k_{\text{det}}k_{\text{osc}}t}$$

so

$$\int_0^{\infty} |f(\tau)| d\tau = F(0) = \frac{1}{k_{\text{det}}k_{\text{osc}}}$$

therefore lock range, for rapidly varying  $\omega_{\text{in}}$ , is

$$\Omega \leq (\pi/2)k_{\text{det}}k_{\text{osc}}$$

(same as slowly-varying lock range . . . )

# PLL: nonlinear analysis

our linear analysis holds as long as

- phase difference stays in the linear range (say,  $\pm 90^\circ$ )
- frequency stays within VCO limits (usually not the problem)

when phase difference moves out of linear range, dynamics of PLL are highly nonlinear, very complex

- analysis of losing and acquiring lock is very difficult
- there is no complete theory or analysis, but lots of practical experience