

# Geometric Programming and Its Applications to EDA Problems

Stephen Boyd

Seung Jean Kim

S. S. Mohan

# Outline

- Basic approach
- Geometric programming & generalized geometric programming
- Digital circuit design applications
- Analog and RF circuit design applications
- Monomial and posynomial fitting
- Conclusions

# Basic Approach

# Basic approach

1. formulate circuit design problem as **geometric program (GP)**, an optimization problem with special form
  2. solve GP using specialized, tailored method
- this tutorial focuses on step 1 (a.k.a. **GP modeling**)
  - step 2 is **technology**

# Why?

- we can solve even large GPs very effectively, using recently developed methods
- so once we have a GP formulation, we can solve circuit design problem effectively

we will see that

- GP is especially good at handling a large number of concurrent constraints
- GP formulation is useful even when it is approximate

# Trade-offs in optimization

- general trade-off between **generality** and **effectiveness**
- generality
  - number of problems that can be handled
  - accuracy of formulation
  - ease of formulation
- effectiveness
  - speed of solution, scale of problems that can be handled
  - global vs. local solutions
  - reliability, baby-sitting, starting point

## Example: least-squares vs. simulated annealing

### least-squares

- large problems reliably (globally) solved quickly
- no initial point, no algorithm parameter tuning
- solves very restricted problem form
- with tricks and extensions, basis of vast number of methods that work (control, filtering, regression, . . . )

### simulated annealing

- can be applied to any problem (more or less)
- slow, needs tuning, babysitting; not global in practice
- method of choice for some problems you can't handle any other way

## Where GP fits in

somewhere in between, closer to least-squares . . .

- like least-squares, large problems can be solved reliably (globally), no starting point, tuning, . . .
- solves a class of problems broader than least-squares, less general than simulated annealing
- **formulation takes effort, but is fun and has high payoff**



# **Geometric Programming & Generalized Geometric Programming**

## Monomial & posynomial functions

$x = (x_1, \dots, x_n)$ : vector of positive optimization variables

- function  $g$  of form

$$g(x) = cx_1^{\alpha_1}x_2^{\alpha_2}\cdots x_n^{\alpha_n},$$

with  $c > 0$ ,  $\alpha_i \in \mathbf{R}$ , is called **monomial**

- sum of monomials, *i.e.*, function  $f$  of form

$$f(x) = \sum_{k=1}^t c_k x_1^{\alpha_{1k}} x_2^{\alpha_{2k}} \cdots x_n^{\alpha_{nk}},$$

with  $c_k > 0$ ,  $\alpha_{ik} \in \mathbf{R}$ , is called **posynomial**

# Examples

with  $x, y, z$  variables,

- $0.23, 2z\sqrt{x/y}, 3x^2y^{-.12}z$  are monomials (hence also posynomials)
- $0.23 + x/y, 2(1 + xy)^3, 2x + 3y + 2z$  are posynomials
- $2x + 3y - 2z, x^2 + \tan x$  are neither

# Generalized posynomials

$f$  is a **generalized posynomial** if it can be formed using addition, multiplication, positive power, and maximum, starting from posynomials

**examples:**

- $\max \{1 + x_1, 2x_1 + x_2^{0.2}x_3^{-3.9}\}$
- $(0.1x_1x_3^{-0.5} + x_2^{1.7}x_3^{0.7})^{1.5}$
- $(\max \{1 + x_1, 2x_1 + x_2^{0.2}x_3^{-3.9}\})^{1.7} + x_2^{1.1}x_3^{3.7}$

# Composition rules

- **monomials** closed under product, division, positive scaling, power, inverse
- **posynomials** closed under sum, product, positive scaling, division by monomial, positive integer power
- **generalized posynomials** closed under sum, product, max, positive scaling, division by monomial, positive power

## Generalized geometric program (GGP)

$$\begin{array}{ll} \text{minimize} & f_0(x) \\ \text{subject to} & f_i(x) \leq 1, \quad i = 1, \dots, m \\ & g_i(x) = 1, \quad i = 1, \dots, p \end{array}$$

$f_i$  are **generalized posynomials**,  $g_i$  are monomials

- called **geometric program (GP)** when  $f_i$  are **posynomials**
- a highly nonlinear constrained optimization problem

## GP example

- maximize volume of box with width  $w$ , height  $h$ , depth  $d$
- subject to limits on wall and floor areas, aspect ratios  $h/w$ ,  $d/w$


$$\begin{aligned} &\text{maximize} && hwd \\ &\text{subject to} && 2(hw + hd) \leq A_{\text{wall}}, \quad wd \leq A_{\text{flr}} \\ &&& \alpha \leq h/w \leq \beta, \quad \gamma \leq d/w \leq \delta \end{aligned}$$

in standard GP form:

$$\begin{aligned} &\text{minimize} && h^{-1}w^{-1}d^{-1} \\ &\text{subject to} && (2/A_{\text{wall}})hw + (2/A_{\text{wall}})hd \leq 1, \quad (1/A_{\text{flr}})wd \leq 1 \\ &&& \alpha h^{-1}w \leq 1, \quad (1/\beta)hw^{-1} \leq 1 \\ &&& \gamma wd^{-1} \leq 1, \quad (1/\delta)w^{-1}d \leq 1 \end{aligned}$$
 
## GGP example: Floor planning

- choose cell widths, heights
- fixed cell areas
- (1 left of 2) above (3 left of 4)
- aspect ratio constraints
- minimize bounding box area



$$\begin{aligned} &\text{minimize} && hw \\ &\text{subject to} && h_i w_i = A_i, \quad 1/\alpha_{\max} \leq h_i/w_i \leq \alpha_{\max}, \\ & && \max\{h_1, h_2\} + \max\{h_3, h_4\} \leq h, \\ & && \max\{w_1 + w_2, w_3 + w_4\} \leq w \end{aligned}$$

... a GGP



## Trade-off analysis


(no equality constraints, for simplicity)

- form perturbed version of original GP, with changed righthand sides:

$$\begin{array}{ll} \text{minimize} & f_0(x) \\ \text{subject to} & f_i(x) \leq u_i, \quad i = 1, \dots, m \end{array}$$

- $u_i > 1$  ( $u_i < 1$ ) means  $i$ th constraint is relaxed (tightened)
- let  $p(u)$  be optimal value of perturbed problem
- plot of  $p$  vs.  $u$  is (globally) **optimal trade-off surface** (of objective against constraints)
 
## Trade-off curves for maximum volume box example



- maximum volume  $V$  vs.  $A_{\text{flr}}$ , for  $A_{\text{wall}} = 100, 1000, 10000$
- $h/w, d/w$  aspect ratio limits 0.5, 2

## Sensitivity analysis

- optimal sensitivity of  $i$ th constraint is

$$S_i = \left. \frac{\partial p/p}{\partial u_i/u_i} \right|_{u=1}$$

- $S_i$  predicts fractional change in optimal objective value if  $i$ th constraint is (slightly) relaxed or tightened
- very useful in practice; give quantitative measure of how tight a binding constraint is
- when we solve a GP **we get all optimal sensitivities at no extra cost**

## Example

- minimize circuit delay, subject to power, area constraints (details later)

$$\begin{array}{ll} \text{minimize} & D(x) \\ \text{subject to} & P(x) \leq P^{\max}, \quad A(x) \leq A^{\max} \end{array}$$

- both constraints tight at optimal  $x^*$ :  $P(x^*) = P^{\max}$ ,  $A(x^*) = A^{\max}$
- suppose optimal sensitivities are  $S^{\text{pwr}} = -2.1$ ,  $S^{\text{area}} = -0.3$
- we predict:
  - for 1% increase in allowed power, optimal delay decreases 2.1%
  - for 1% increase in allowed area, optimal delay decreases 0.3%

## GP and GGP attributes

- after log transform of variables/constraints, they become **convex problems**
- can convert GGP to GP, *e.g.*,  $f(x) + \max\{g(x), h(x)\} \leq 1$  becomes

$$f(x) + t \leq 1, \quad g(x)/t \leq 1, \quad h(x)/t \leq 1$$

where  $t$  is new (dummy) variable

- **conversion tricks can be automated**
  - parser scans problem description, forms GP
  - efficient GP solver solves GP
  - solution transformed back (dummy variables eliminated)

# How GPs are solved

the practical answer: **none of your business**

more politely: **you don't need to know**

it's **technology**:

- good algorithms are known
- good software implementations are available

## How GPs are solved

- work with log of variables:  $y_i = \log x_i$
- take log of monomials/posynomials to get

$$\begin{aligned} & \text{minimize} && \log f_0(e^y) \\ & \text{subject to} && \log f_i(e^y) \leq 0, \quad i = 1, \dots, m \\ & && \log g_i(e^y) = 0, \quad i = 1, \dots, p \end{aligned}$$

- $\log f_i(e^y)$  are (smooth) **convex** functions
- $\log g_i(e^y)$  are affine functions, *i.e.*, linear plus a constant
- solve (nonlinear) **convex optimization problem** above using interior-point method

## Current state of the art

- basic interior-point method that exploits sparsity, generic GP structure
  - approaching efficiency of linear programming solver
    - sparse 1000 vbles, 10000 monomial terms: few seconds
    - sparse 10000 vbles, 100000 monomial terms: minute
    - sparse  $10^6$  vbles,  $10^7$  monomial terms: hour
- (these are order-of-magnitude estimates, on simple PC)



# History

- GP (and term 'posynomial') introduced in 1967 by Duffin, Peterson, Zener
- engineering applications from the very beginning
  - early applications in chemical, mechanical, power engineering
  - digital circuit transistor and wire sizing with Elmore delay since 1984 (Fishburn & Dunlap's TILOS)
  - analog circuit design since 1997 (Hershenson, Boyd, Lee)
  - other applications in finance, wireless power control, statistics, . . .
- extremely efficient solution methods since 1994 or so (Nesterov & Nemirovsky)


## Mixed-integer geometric program

$$\begin{aligned} & \text{minimize} && f_0(x) \\ & \text{subject to} && f_i(x) \leq 1, \quad i = 1, \dots, m \\ & && g_i(x) = 1, \quad i = 1, \dots, p \\ & && x_i \in \mathcal{D}_i, \quad i = 1, \dots, k \end{aligned}$$

- $f_i$  are generalized posynomials,  $g_i$  are monomials
- $\mathcal{D}_i$  are discrete sets, *e.g.*,  $\{1, 2, 3, 4, \dots\}$  or  $\{1, 2, 4, 8 \dots\}$
- **very hard** to solve exactly; all methods make some compromise (compared to methods for GP)
- **heuristic methods** attempt to find good approximate solutions quickly, but cannot guarantee optimality
- **global methods** always find the global solution, but can be extremely slow


# **Digital Circuit Design Applications**

# Gate scaling

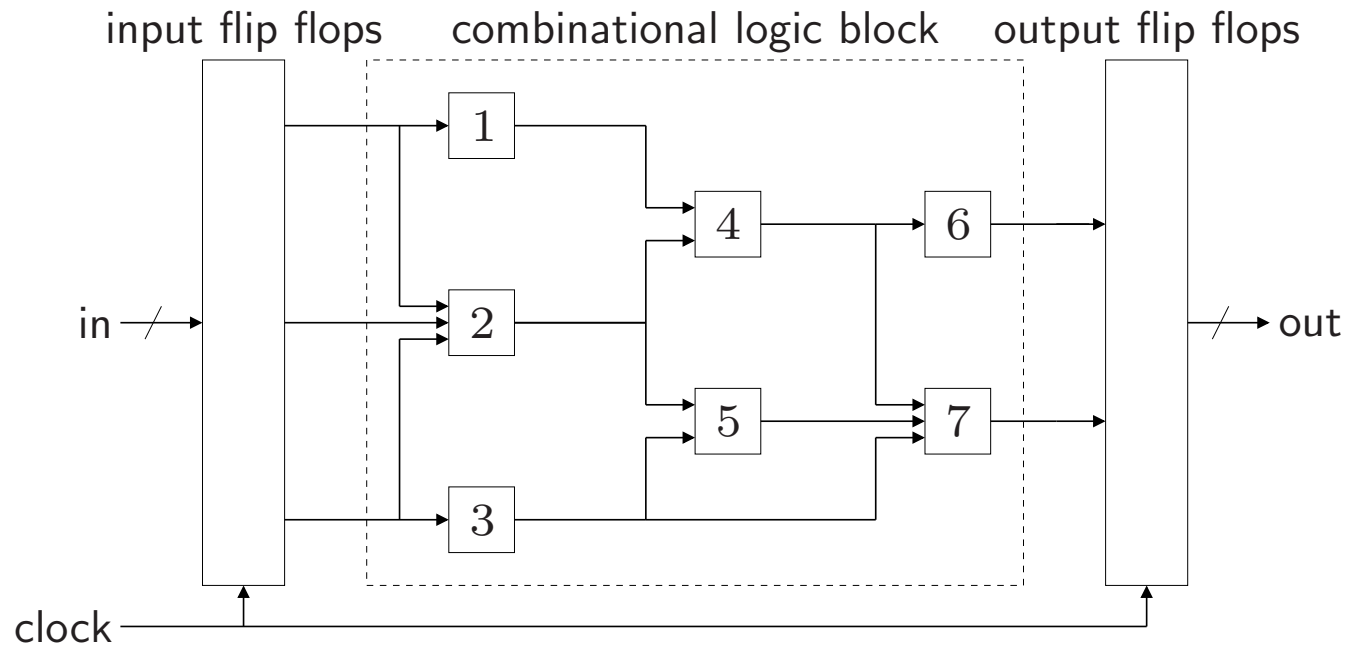

- combinational logic; circuit topology & gate types given
- gate sizes (scale factors  $x_i \geq 1$ ) to be determined
- scale factors affect total circuit area, power and delay

## RC gate delay model

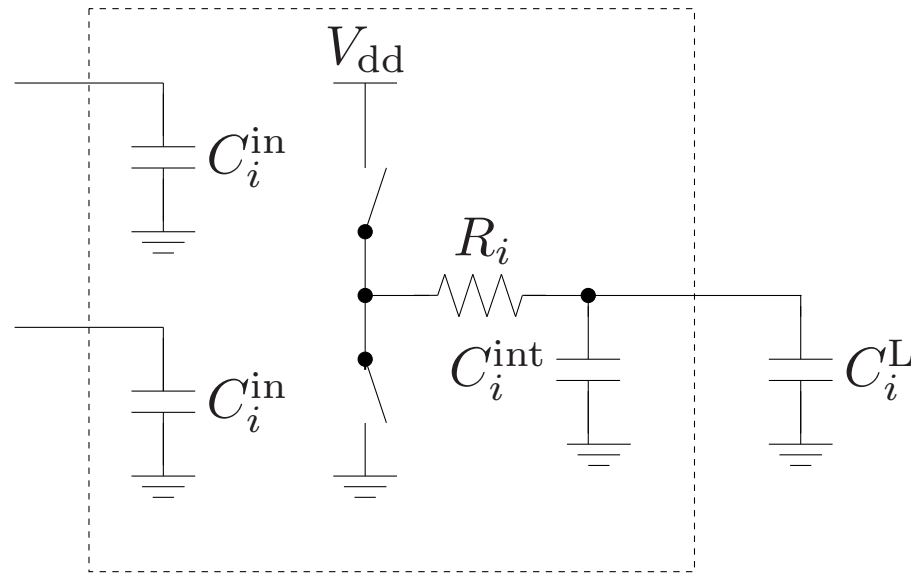

- input & intrinsic capacitances, driving resistance, load capacitance

$$C_i^{in} = \bar{C}_i^{in} x_i, \quad C_i^{int} = \bar{C}_i^{int} x_i, \quad R_i = \bar{R}_i / x_i, \quad C_i^L = \sum_{j \in \text{FO}(i)} C_j^{in}$$


## RC gate model

- RC gate delay:

$$D_i = 0.69R_i(C_i^L + C_i^{\text{int}}) = 0.69 \left( \bar{R}_i \bar{C}_i^{\text{in}} + (\bar{R}_i/x_i) \sum_{j \in \text{FO}(i)} \bar{C}_j^{\text{in}} x_j \right)$$

- $D_i$  are **posynomials** (of scale factors)

## Path and circuit delay

 

- delay of a path: sum of delays of gates on path  
... **posynomial**
- circuit delay: maximum delay over all paths  
... **generalized posynomial**

## Area & power

- total circuit area:  $A = x_1 \bar{A}_1 + \cdots + x_n \bar{A}_n$

- total power is  $P = P_{\text{dyn}} + P_{\text{stat}}$

- dynamic power  $P_{\text{dyn}} = \sum_{i=1}^n f_i (C_i^{\text{L}} + C_i^{\text{int}}) V_{\text{dd}}^2$

$f_i$  is gate switching frequency

- static power  $P_{\text{stat}} = \sum_{i=1}^n x_i \bar{I}_i^{\text{leak}} V_{\text{dd}}$

$\bar{I}_i^{\text{leak}}$  is leakage current (average over input states) of unit scaled gate

- $A$  and  $P$  are linear functions of  $x$ , with positive coefficients, hence posynomials



## Basic gate scaling problem

$$\begin{array}{ll} \text{minimize} & D \\ \text{subject to} & P \leq P^{\max}, \quad A \leq A^{\max} \\ & 1 \leq x_i, \quad i = 1, \dots, n \end{array}$$

... a **GGP**

extensions/variations:

- minimize area, power, or some combination
- maximize clock frequency subject to area, power limits
- add other constraints
- optimal trade-off of area, power, delay

## Clock frequency maximization

- $f_{\text{clk}}$  is variable
- timing requirement:  $D \leq 0.8/f_{\text{clk}}$   
(20% margin for flip-flop delay, setup time, clock skew . . . )
- $P$  is posynomial of scalings and  $f_{\text{clk}}$ , assuming  $f_i$  scale with  $f_{\text{clk}}$

$$\begin{array}{ll} \text{maximize} & f_{\text{clk}} \\ \text{subject to} & P \leq P^{\max}, \quad A \leq A^{\max}, \quad (1/0.8)Df_{\text{clk}} \leq 1, \\ & 1 \leq x_i, \quad i = 1, \dots, n \end{array}$$

. . . a **GGP**

## Example: 32-bit Ladner-Fisher adder


- 451 gates (scale factors), 5 gate types, 64 inputs, 32 outputs
- logical effort gate delay model parameters:

gate type	$\bar{C}^{\text{in}}$	$\bar{C}^{\text{int}}$	$\bar{R}$	$\bar{A}$	$\bar{I}^{\text{leak}}$
INV	3	3	0.48	3	0.006
NAND2	4	6	0.48	8	0.007
NOR2	5	6	0.48	10	0.009
AOI21	6	7	0.48	17	0.003
OAI21	6	7	0.48	16	0.003

- time unit is  $\tau$ , delay of min-size inverter ( $0.69 \cdot 0.48 \cdot 3 = 1$ )
- area (total width) unit is width of NMOS in min-size inverter

 
## Example: 32-bit Ladner-Fisher adder

- typical optimization time: few seconds on PC


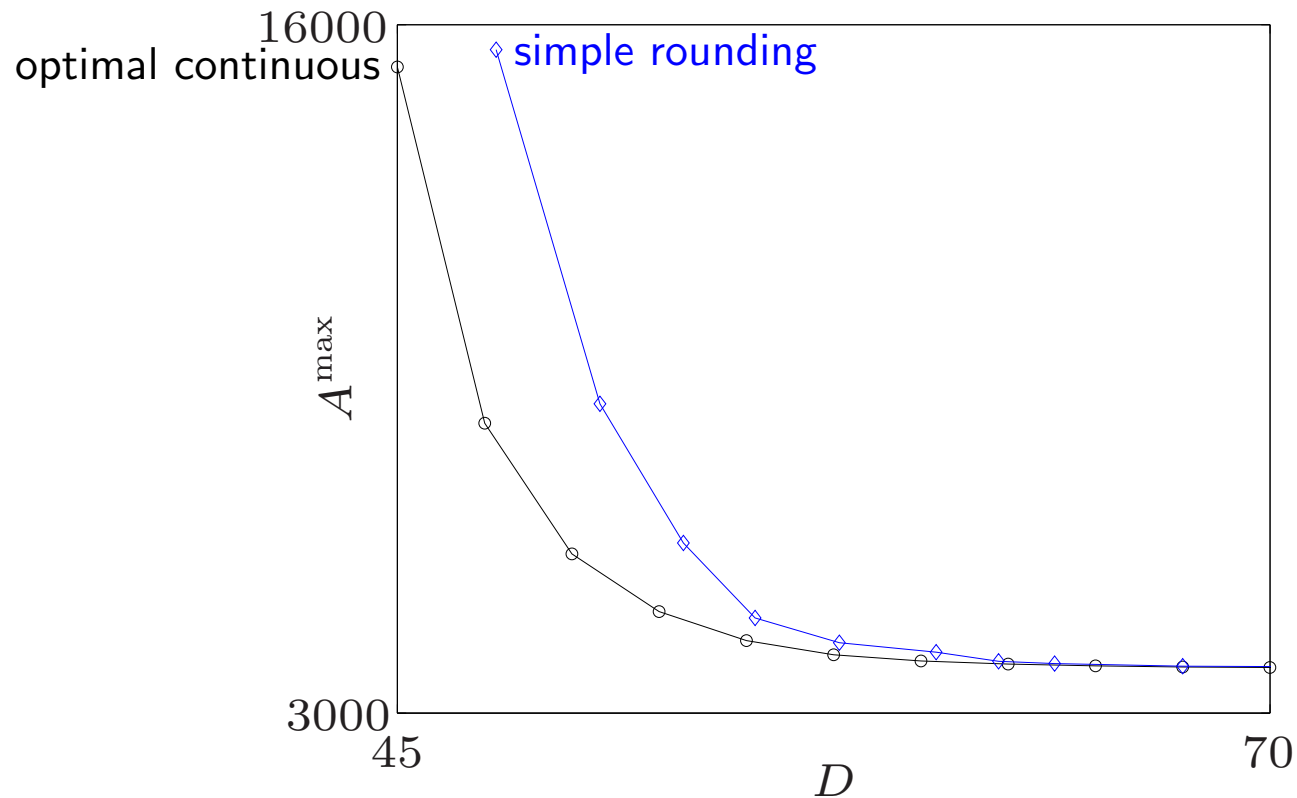
## 32-bit Ladner-Fisher adder with discrete scale factors

- add constraints  $x_i \in \{1, 2, 4, 8, 16, \dots\}$
- simple rounding of optimal continuous scalings



## Sparse GP gate scaling problem

$$\begin{aligned} & \text{minimize} && D \\ & \text{subject to} && T_j \leq D \quad \text{for } j \text{ an output gate} \\ & && T_j + D_i \leq T_i \quad \text{for } j \in \text{FI}(i) \\ & && P \leq P^{\max}, \quad A \leq A^{\max} \\ & && 1 \leq x_i, \quad i = 1, \dots, n \end{aligned}$$

- $T_i$  are upper bounds on signal arrival times
- **extremely sparse GP**; can be solved very efficiently

## Better (generalized posynomial) models

can greatly improve model, while retaining GP compatibility  
(hence efficient global solution)

- area, delay, power can be any generalized posynomials of scale factors,  
*e.g.*,

$$D_i = a_i + b_i(C_i^L)^{1.05}x_i^{-0.9}, \quad P_i = c_i + d_i(C_i^L)^{1.2} + e_ix_i^{1.1}$$

- these can be found by more refined analysis, or fitting generalized posynomials to simulation/characterization data

## Distinguishing gate transitions

- can distinguish rising and falling transitions, with different delay, energy,  $C^{\text{in}}$ , for each gate input/transition
- (bounds on) signal arrival times can be propagated through recursions, *e.g.*,

$$T_i^{\text{r}} = \max_{j \in \text{FI}(i)} \{T_j^{\text{r}} + D_{ji}^{\text{rr}}, T_j^{\text{f}} + D_{ji}^{\text{fr}}\}, \quad T_i^{\text{f}} = \max_{j \in \text{FI}(i)} \{T_j^{\text{r}} + D_{ji}^{\text{rf}}, T_j^{\text{f}} + D_{ji}^{\text{ff}}\}$$

- gate scaling problem more complex, but **still a GGP**  
(hence can be efficiently solved)



## Modeling signal slopes

- associate (worst-case) output signal transition time  $\tau$  with each gate
- model delay, energy, input capacitance as (generalized posynomial) functions of scale factor, load capacitance, input transition time
- propagate output transition time using (generalized posynomial) function of scale factor, load capacitance, input transition time
- common model:

$$D_i = a_i C_i^L / x_i + \kappa_i \tau_i^{\text{in}}, \quad E_i = b_i (C_i^L + c_i x_i) + \lambda_i x_i \tau_i^{\text{in}}, \quad \tau_i = \nu_i D_i$$

- gate scaling problem **still a GGP**

## Design with a standard library

- circuit topology is fixed; choose size for each gate from **discrete library**
- a combinatorial optimization problem, difficult to solve exactly
- GP approach
  - for each gate type in library, fit given library data to find GP-compatible models of delay, power, . . .
  - size with **continuous** fitted models, using GP
  - snap continuous scale factors back to standard library

## Robust design over corners

- have  $K$  corners or scenarios, *e.g.*, combinations of
  - process parameters (channel length, oxide thickness, . . . )
  - environmental parameters (supply voltage, temperature, . . . )
- for each corner have (slightly) different models for delay, power, . . .
- **robust design** finds gate scalings that work well for **all corners**

## Robust design over corners

- basic (worst-case) robust design over corners:

$$\begin{aligned} \text{minimize} \quad & D^{\text{wc}} = \max\{D^{(1)}, \dots, D^{(K)}\} \\ \text{subject to} \quad & P^{(1)}(x) \leq P^{\text{max}}, \dots, P^{(K)}(x) \leq P^{\text{max}} \\ & A \leq A^{\text{max}} \\ & 1 \leq x_i, \quad i = 1, \dots, n \end{aligned}$$

- many variations, *e.g.*, minimize average delay over corners,

$$D^{\text{avg}} = (1/K) \left( D^{(1)} + \dots + D^{(K)} \right)$$

- results in (very large, but sparse) **GGP**

## Multiple-scenario design

- have  $K$  scenarios or operating modes, with  $K$  models for  $P$ ,  $D$ , . . .
- scenarios are combinations of
  - supply & threshold voltages
  - clock frequency
  - specifications & constraints
- like corner-based robust design, but scenarios are **intentional**
- find one set of gate scalings that work well in all scenarios

## Example


- find single set of gate scalings to support both high performance mode and low power mode
  - in high performance mode:  $P^{\text{fast}} \leq \bar{P}^{\text{fast}}, D^{\text{fast}} \leq \bar{D}^{\text{fast}}$
  - in low power mode:  $P^{\text{slow}} \leq \bar{P}^{\text{slow}}, D^{\text{slow}} \leq \bar{D}^{\text{slow}}$

$$\begin{array}{ll} \text{minimize} & A \\ \text{subject to} & P^{\text{slow}} \leq \bar{P}^{\text{slow}}, \quad D^{\text{slow}} \leq \bar{D}^{\text{slow}} \\ & P^{\text{fast}} \leq \bar{P}^{\text{fast}}, \quad D^{\text{fast}} \leq \bar{D}^{\text{fast}} \\ & 1 \leq x_i, \quad i = 1, \dots, n \end{array}$$

... a GGP
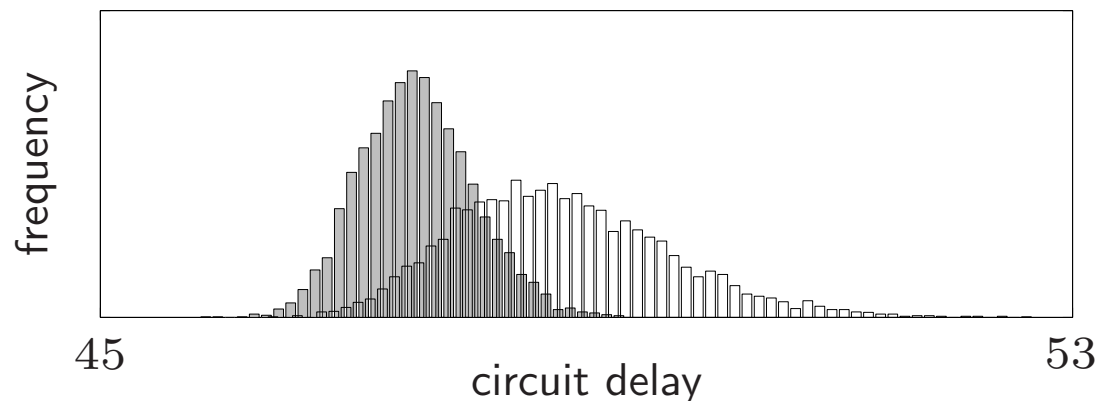
## Statistical parameter variation

- circuit performance depends on random device and process parameters
- hence, performance measures like  $P$ ,  $D$  are random variables  $\mathbf{P}$ ,  $\mathbf{D}$
- delay  $\mathbf{D}$  is max of many random variables; often skewed to right
- **distributions** of  $\mathbf{P}$ ,  $\mathbf{D}$  depend on gate scalings  $x_i$



- related to (parametric) yield, DFM, DFY . . .

## Statistical design

- measure random performance measures by 95% quantile (say)

$$\begin{array}{ll} \text{minimize} & \mathbf{Q}^{.95}(\mathbf{D}) \\ \text{subject to} & \mathbf{Q}^{.95}(\mathbf{P}) \leq P^{\max}, \quad A \leq A^{\max} \\ & 1 \leq x_i, \quad i = 1, \dots, n \end{array}$$

- **extremely difficult** stochastic optimization problem; almost no analytic/exact results
- but, (GP-compatible) heuristic method works well



## Statistical model

- for simplicity consider  $V_{th}$  variation only
- Pelgrom's model:  $\sigma_{V_{th}} = \bar{\sigma}_{V_{th}} x^{-1/2}$
- alpha-power law model:  $D \propto V_{dd}/(V_{dd} - V_{th})^\alpha$ , with  $\alpha \approx 1.3$
- for small variation in  $V_{th}$ ,

$$\sigma_D \approx \left| \frac{\partial D}{\partial V_{th}} \right| \sigma_{V_{th}} = \alpha (V_{dd} - V_{th})^{-1} \bar{\sigma}_{V_{th}} x^{-0.5} D$$

- $\sigma_D$  is posynomial
- get similar (posynomial) models for  $\sigma_D$  with more complex gate delay statistical models

## Heuristic for statistical design

- assume generalized posynomial models for gate delay mean  $D_i(x)$  and variance  $\sigma_i(x)^2$
- optimize using **surrogate gate delays**

$$\tilde{D}_i(x) = D_i(x) + \kappa_i \sigma_i(x)$$


$\kappa_i \sigma_i(x)$  are **margins** on gate delays ( $\kappa_i$  is typically 2 or 3)

- verify statistical performance via Monte Carlo analysis  
(can update  $\kappa_i$ 's and repeat)

 
# Heuristic for statistical design

heuristic statistical design

- often far superior to design obtained ignoring statistical variation
- not very sensitive to details of process variation statistics (distribution shape, correlations, . . . )
- below: 32-bit Ladner-Fisher adder, Pelgrom variance model


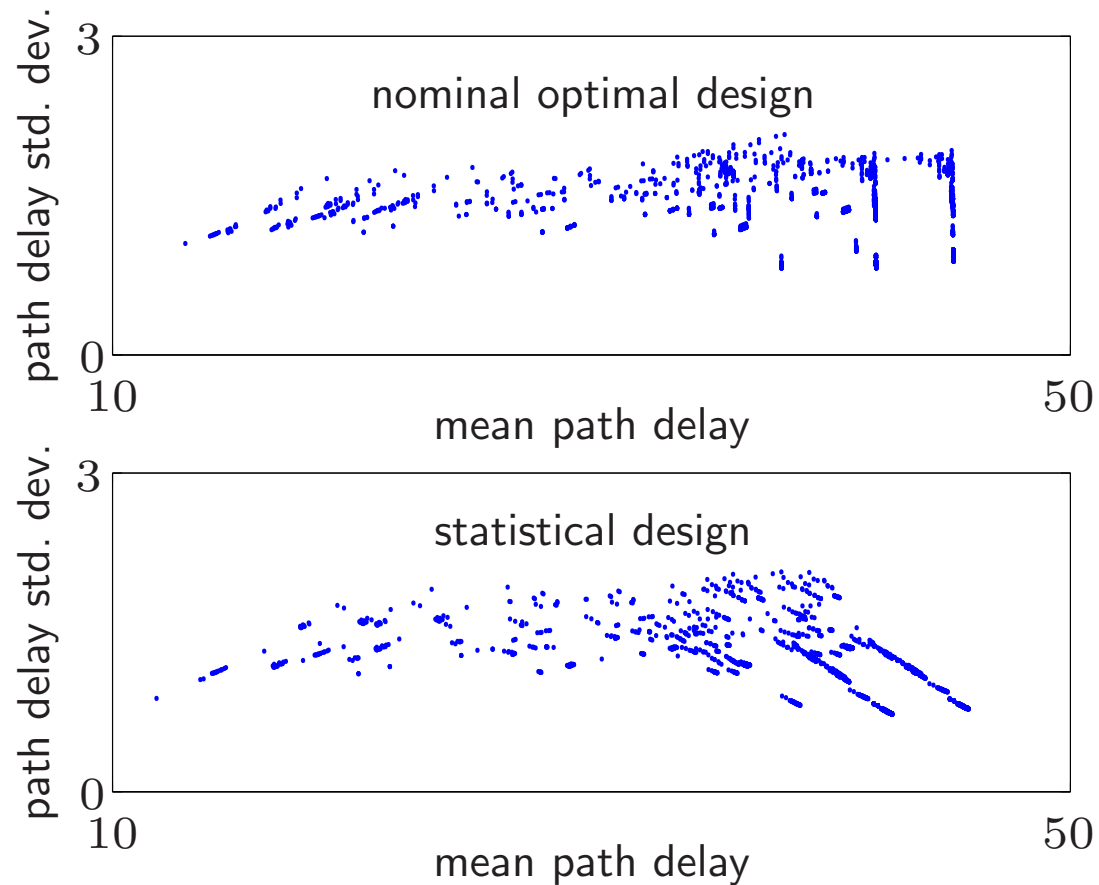
## Path delay mean/std. dev. scatter plots



# Joint size and supply/threshold voltage optimization

- **goal:** jointly optimize gate size, supply and threshold voltages via GGP
- **need to:** model delay, power as generalized posynomial functions of gate size, supply and threshold voltages

## Generalized posynomial delay model

- alpha-power law model predicts variation in gate delay with  $V_{dd}$ ,  $V_{th}$ :

$$D_i = \frac{V_{dd,i}}{(V_{dd,i} - V_{th,i})^\alpha} \tilde{D}_i(x)$$

$\tilde{D}_i$  is generalized posynomial gate delay model, function of scalings  $x$

- generalized posynomial approximation

$$\hat{D}_i = V_{dd,i}^{1-\alpha} (1 + V_{th,i}/V_{dd,i} + \cdots + (V_{th,i}/V_{dd,i})^5)^\alpha \tilde{D}_i(x)$$

error under 1% for  $V_{dd,i} \geq 2V_{th,i}$ ,  $1.3 \leq \alpha \leq 2$

## Generalized posynomial power model

- gate dynamic power:  $P_{\text{dyn}} = \sum_{i=1}^n f_i(C_i^L + C_i^{\text{int}})V_{\text{dd},i}^2$

- simple static power model:



$$P_{\text{stat}} = \sum_{i=1}^n x_i \bar{I}_i^{\text{leak}} V_{\text{dd},i}, \quad \bar{I}_i^{\text{leak}} \propto e^{-(V_{\text{th},i} - \gamma V_{\text{dd},i})/V_0}$$

$\gamma, V_0$  are (process) constants

- $P_{\text{stat}}$  (by itself) **cannot** be approximated well by a generalized posynomial over large range of  $V_{\text{dd}}, V_{\text{th}}$
- but, total power  $P = P_{\text{dyn}} + P_{\text{stat}}$  **can** be approximated well by a generalized posynomial
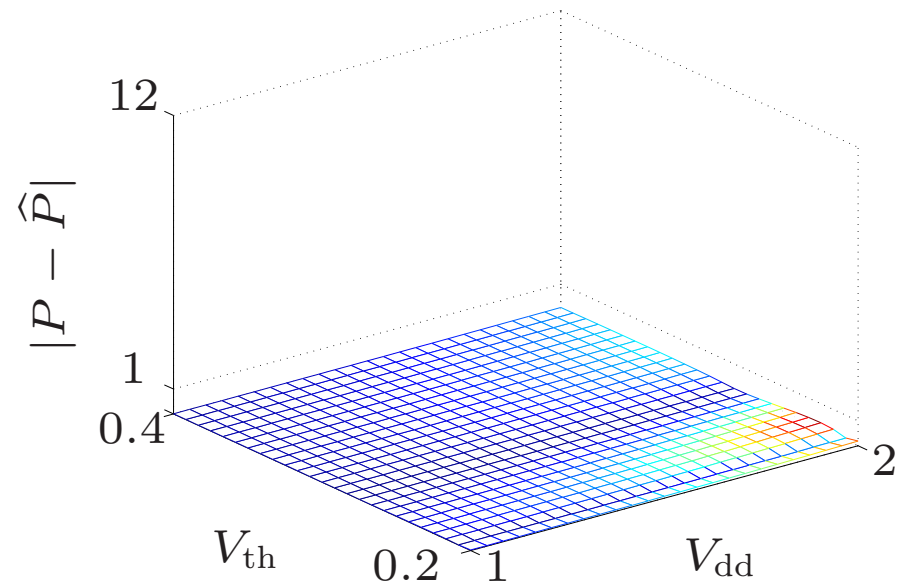 
## Generalized posynomial power model example

total power  $P = V_{\text{dd}}^2 + 30V_{\text{dd}}e^{-(V_{\text{th}} - 0.06V_{\text{dd}})/0.039}$  (up to scaling)



- generalized posynomial approximation

$$\hat{P} = V_{\text{dd}}^2 + 0.06V_{\text{dd}}(1 + 0.0031V_{\text{dd}})^{500}(V_{\text{th}}/0.039)^{-6.16}$$

- error under 3% (well under accuracy of model!)



## Joint optimization of gate sizes, $V_{dd}$ , & $V_{th}$

basic problem, with variables:  $x_i, V_{th,i}, V_{dd,i}$

$$\begin{aligned} &\text{minimize} && D \\ &\text{subject to} && P \leq P^{\max}, \quad A \leq A^{\max} \\ & && V_{th}^{\min} \leq V_{th,i} \leq V_{th}^{\max}, \quad i = 1, \dots, n \\ & && V_{dd}^{\min} \leq V_{dd,i} \leq V_{dd}^{\max}, \quad i = 1, \dots, n \\ & && \text{other constraints} \dots \end{aligned}$$

(... a **GGP**)

discrete allowed  $V_{dd}, V_{th}$  values yields MIGP

## Extensions/variations

- clustering, with single  $V_{dd}$ ,  $V_{th}$  per cluster:

$$V_{dd,i} = V_{dd,j}, \quad V_{th,i} = V_{th,j} \quad \text{for } i, j \text{ in same cluster}$$

... monomial (equality) constraints

- clustered voltage scaling (CVS): low  $V_{dd}$  cells cannot drive high  $V_{dd}$  cells

$$V_{dd,j} \leq V_{dd,i} \quad \text{for } j \in \text{FO}(i)$$

... monomial (inequality) constraints


- multimode design: choose single set of gate scalings, different  $V_{dd}^{(k)}$ ,  $V_{th}^{(k)}$  for each scenario  $k = 1, \dots, K$

related to **dynamic voltage scaling**, **adaptive bulk biasing**, ...


## Joint optimization examples

- Ladner-Fisher adder
- variables: gate scalings  $x_i$ , supply voltages  $V_{dd,i}$ , threshold voltages  $V_{th,i}$
- four delay-power trade-off curves:
  - fixed  $V_{dd,i} = 1.0$ , fixed  $V_{th,i} = 0.3$
  - fixed  $V_{dd,i} = 1.0$ , variable  $V_{th,i} \in \{0.2, 0.3, 0.4\}$
  - CVS with  $V_{dd,i} \in \{0.6, 1.0\}$ ,  $V_{th,i} \in \{0.2, 0.3, 0.4\}$
  - variable continuous  $V_{dd}$ ,  $V_{th}$ ,  $0.6 \leq V_{dd,i} \leq 1.0$ ,  $0.2 \leq V_{th,i} \leq 0.4$   
(not practical, but serves as lower bound)


# Trade-off curve analysis

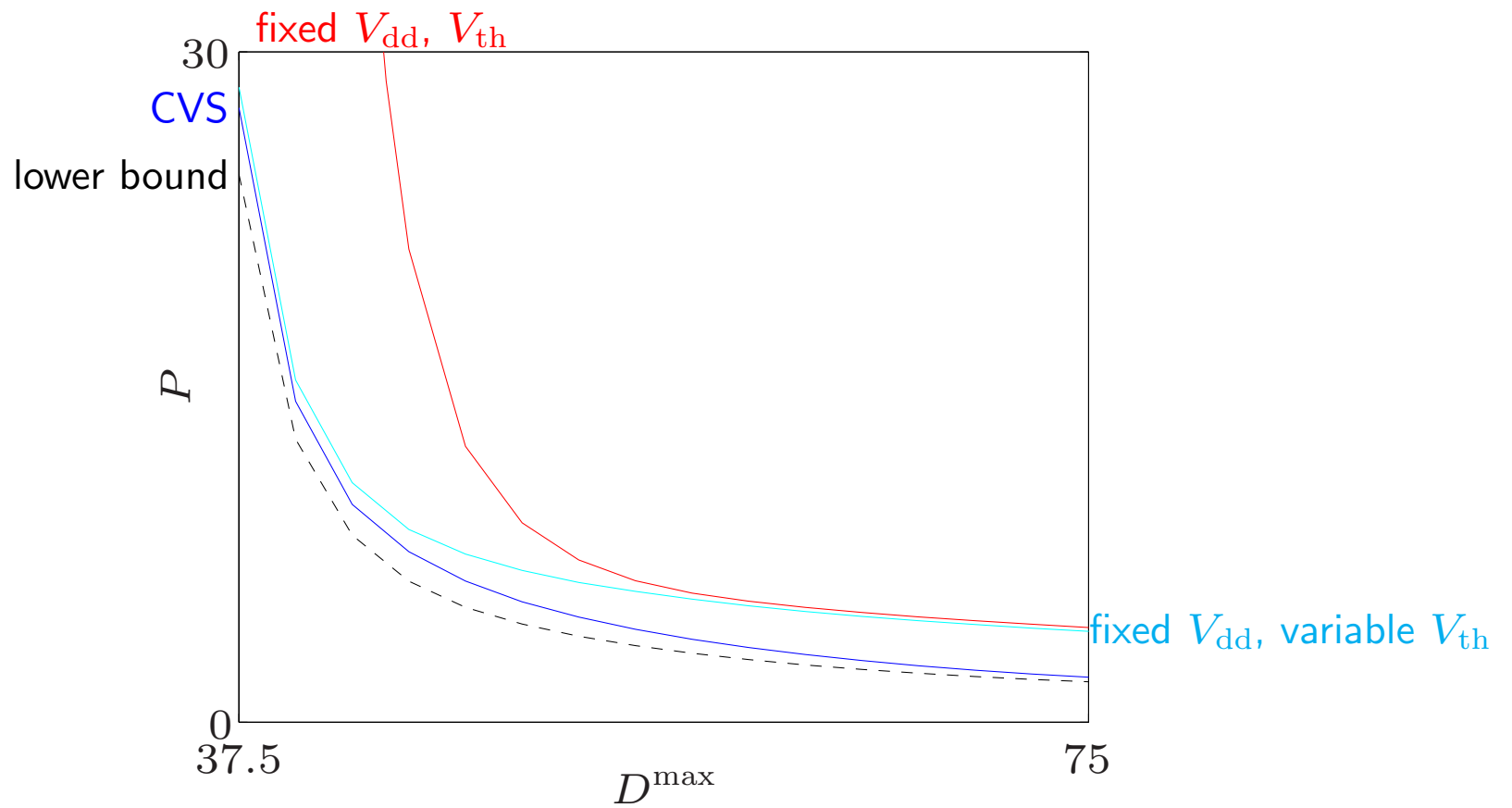
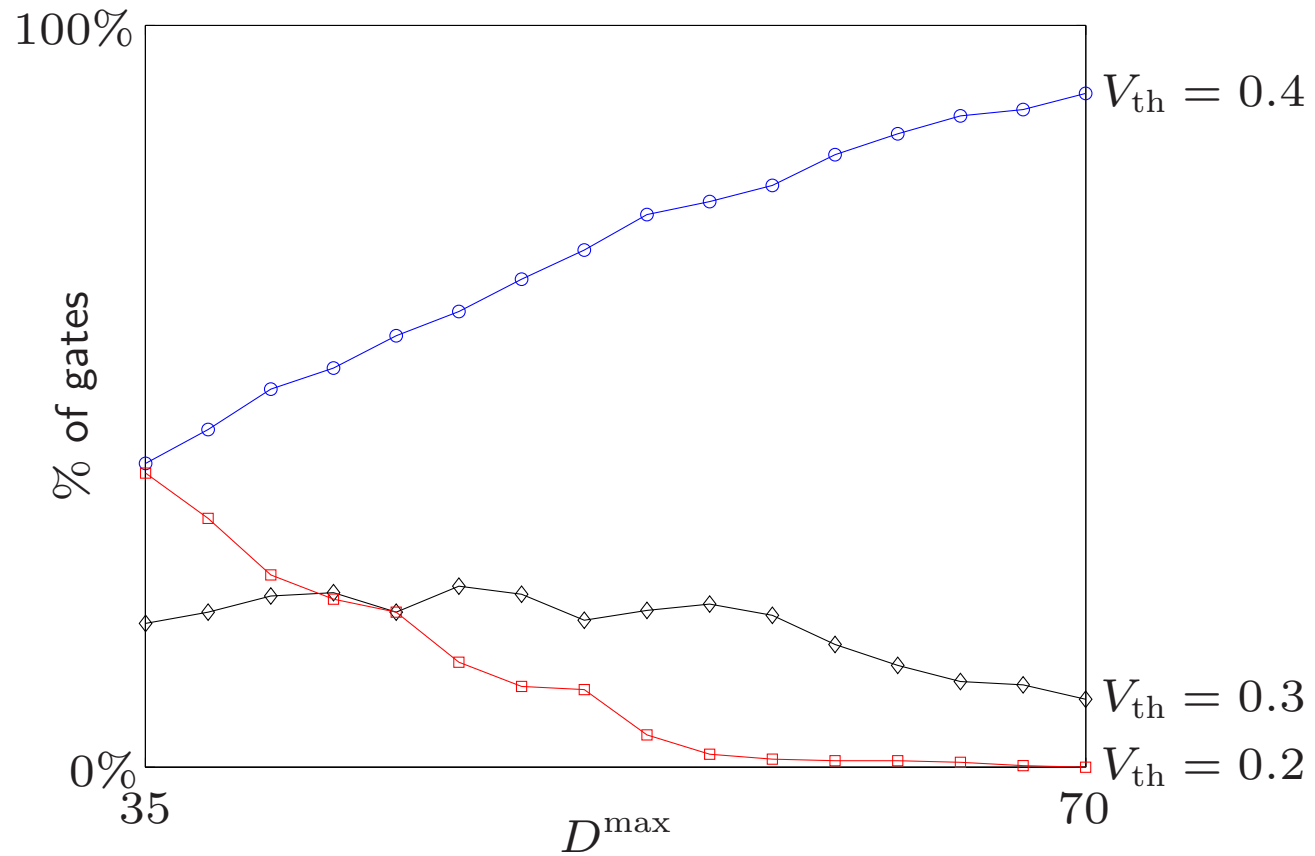
# Design with multiple threshold voltages




# Clustered voltage scaling

 

# Wire and device sizing

RC tree:

 


- $R_i$ s and  $C_i$ s are generalized posynomials of some underlying variables  $x$

## Elmore delay

- **Elmore delay** at node  $i$ :

$$D_i = \int_0^{\infty} v_i(t) dt$$

 area under voltage curve, when voltages are initialized as  $v_i(0) = 1$



- Elmore delay of RC tree is  $D = \max\{D_1, \dots, D_N\}$



## Elmore delay expression

- analytic expression for Elmore delay  $D_i$

$$D_i = \sum_{j \in \mathbf{P}(i)} R_j C_j^{\text{tot}}$$

- $\mathbf{P}(i)$  is path from root to node  $i$
- $C_i^{\text{tot}}$  is the total capacitance downstream from node  $i$  (including  $C_i$ )
- $D_i$  is **posynomial** of  $x$
- $D$  is **generalized posynomial** of  $x$

## RC tree optimization

- minimize RC tree delay subject to (generalized posynomial) constraints

$$\begin{array}{ll} \text{minimize} & D \\ \text{subject to} & f_i(x) \leq 0, \quad i = 1, \dots, m \end{array}$$


... a **GGP**

- sparse formulation:



$$\begin{array}{ll} \text{minimize} & s \\ \text{subject to} & s \geq D_i, \quad i = 1, \dots, n \\ & C_j^{\text{tot}} \geq \sum_{i \in \text{Child}(j)} C_i^{\text{tot}} + C_j, \quad i = 1, \dots, n \\ & D_i \geq D_{\text{Par}(k)} + R_i C_i^{\text{tot}}, \quad i = 1, \dots, n \\ & f_i(x) \leq 0, \quad i = 1, \dots, m \end{array}$$
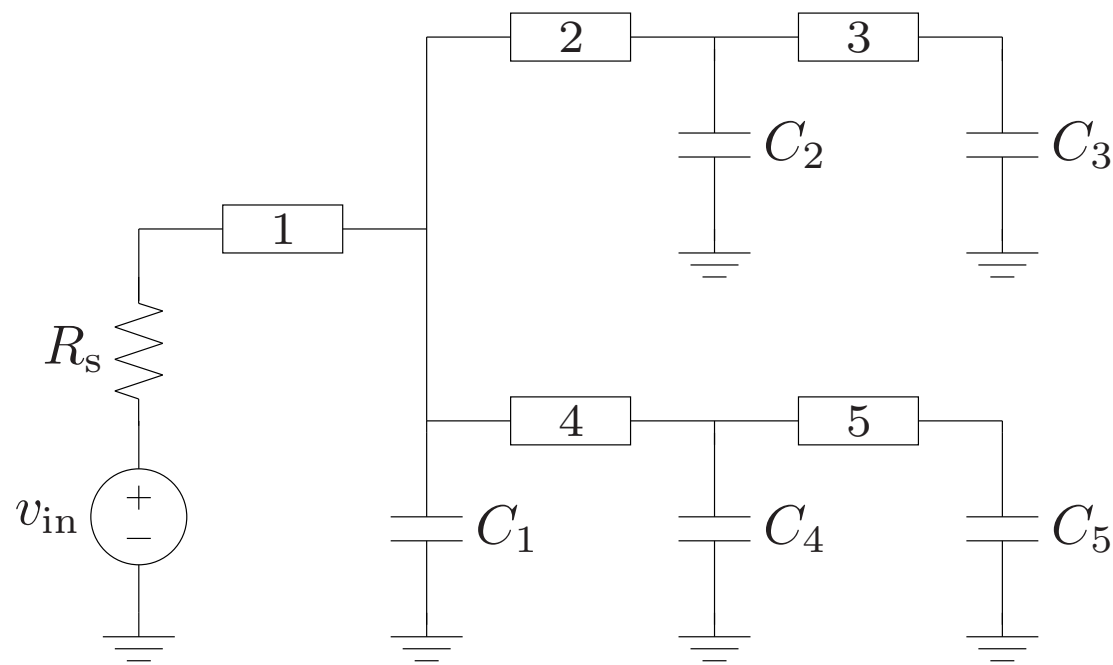
# Wire sizing

- choose wire segment widths  $w_i, \dots, w_N$  in an interconnect network
- optimize delay, area



## $\pi$ model for wire segment

  

- wire resistance and capacitances

$$R_i = \alpha_i \frac{l_i}{w_i}, \quad \bar{C}_i = \beta_i l_i w_i + \gamma_i l_i,$$

- with  $\pi$  model, interconnect network becomes RC tree, with  $R_i$ s and  $C_i$ s posynomial functions of wire segment widths  $w_i$

## Wire sizing via GP

$$\begin{array}{ll} \text{minimize} & D \\ \text{subject to} & w_i^{\min} \leq w_i \leq w_i^{\max}, \quad i = 1, \dots, N \\ & l_1 w_1 + \dots + l_N w_N \leq A^{\max} \end{array}$$


... a GGP

- can easily optimize interconnect network with 10000 wires, using sparse GP formulation
- can use more accurate generalized posynomial models of  $R_i, C_i$

## Device sizing


- devices (and wire segments) are sized individually
- replace each device with switch-level RC model
- each transition is associated with RC tree
- use Elmore delay to measure delay of transition
- . . . **problem is GGP**

## Switch-level RC device model

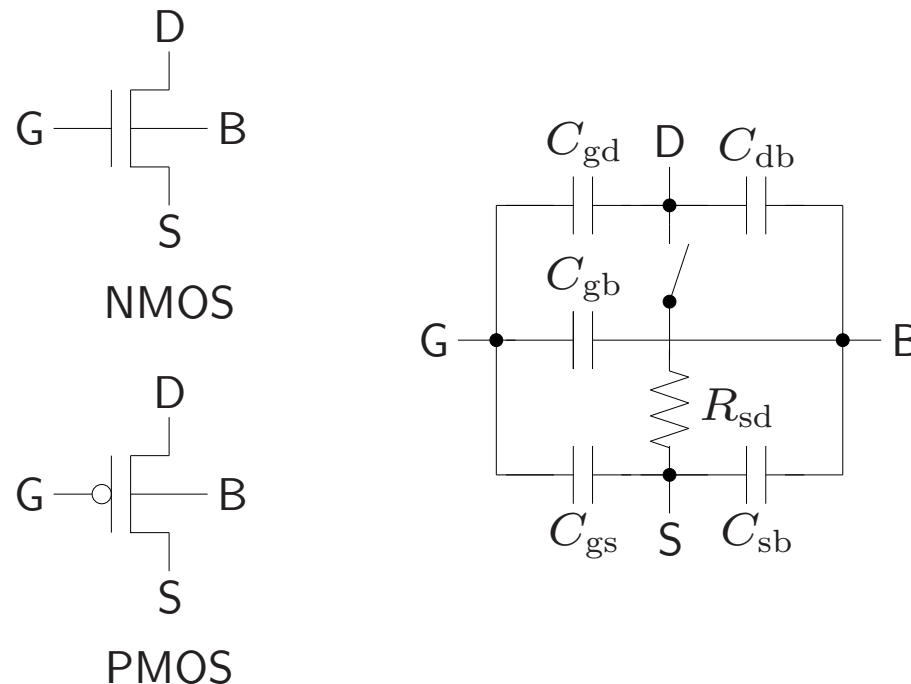

- crude linear approximation of device, for delay and power optimization
- $R$ , all  $C$ s are generalized posynomials of device width
- we'll ignore  $C_{gd}$  (but can be incorporated via Miller effect . . . )

## Example: 2-input NAND

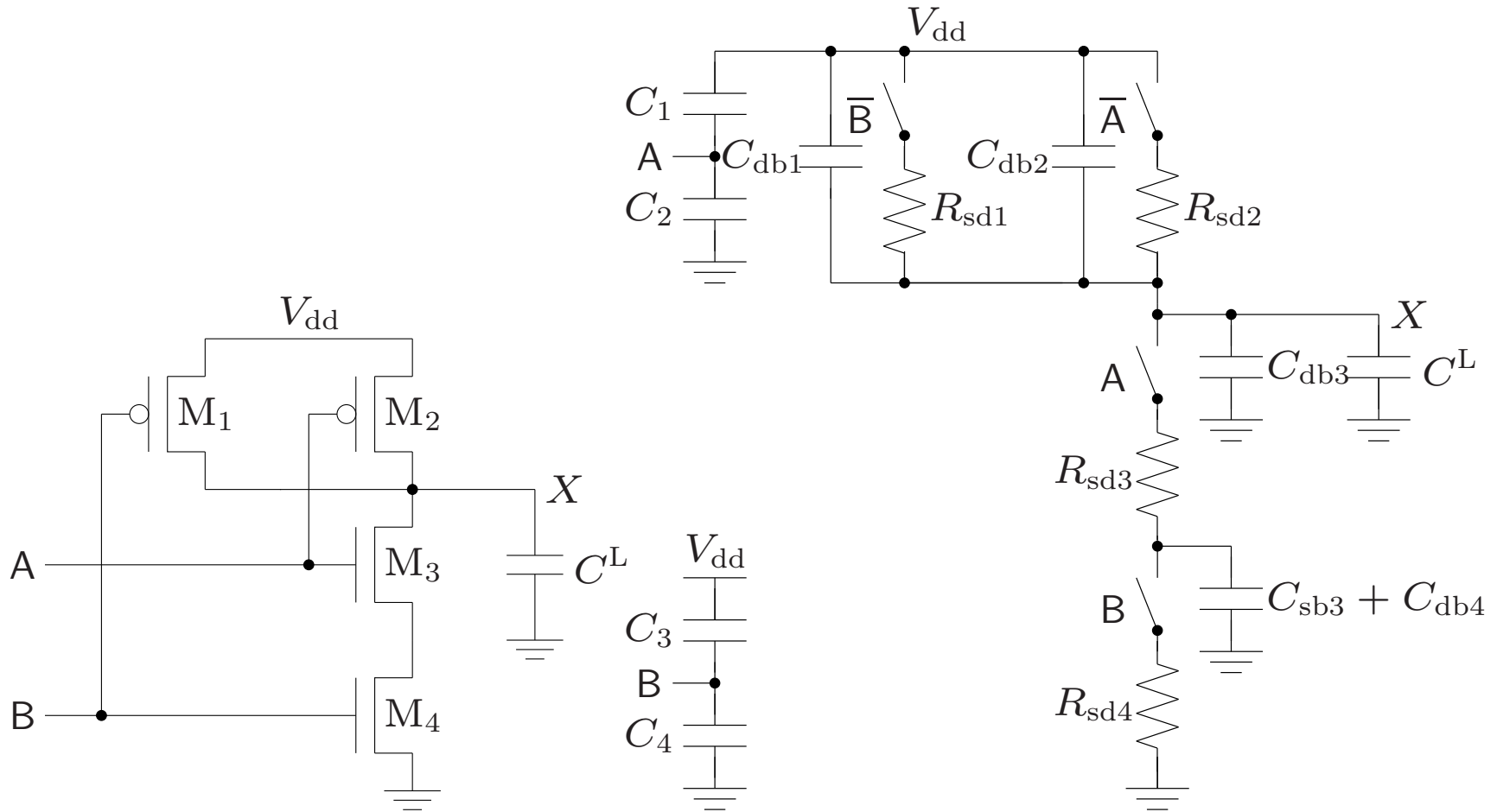


$$C_1 = C_{gb2} + C_{gs2}, \quad C_2 = C_{gb3} + C_{gs3}, \quad C_3 = C_{gb1} + C_{gs1}, \quad C_4 = C_{gb4} + C_{gs4}$$


 
## Example transition

- transition: B falls from  $V_{dd}$  to zero; A remains at  $V_{dd}$
- associated RC tree:




$$C_1 = C_{db1} + C_{db2} + C_{db3}, \quad C_2 = C_{sb3} + C_{db4}$$

- Elmore delay:  $D = R_{sd1}(C^L + C_1 + C_2)$
- energy lost:  $E = (C^L + C_1 + C_2)V_{dd}^2/2$


# **Analog and RF Circuit Design Applications**

## Large signal MOS model

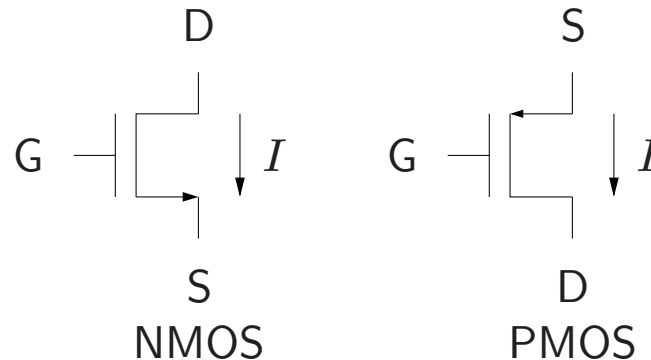

- gate overdrive voltage  $V_{\text{gov}} = V_{\text{gs}} - V_{\text{th}}$
- saturation condition:  $V_{\text{ds}} \geq V_{\text{dsat}} = V_{\text{gov}}$  ( $V_{\text{dsat}}$  is minimum drain-source voltage for device to operate in saturation)
- square-law model  $I = 0.5\mu C_{\text{ox}}(W/L)V_{\text{gov}}^2$
- GP model variables:  $I$ ,  $L$ ,  $W$
- $V_{\text{gov}} = (\mu C_{\text{ox}}/2)^{-1/2}I^{1/2}L^{1/2}W^{-1/2}$  is monomial
- $V_{\text{gs}} = V_{\text{gov}} + V_{\text{th}}$  is posynomial

## Small signal dynamic MOS model

 

- transconductance  $g_m = (2\mu C_{ox})^{1/2} I^{1/2} L^{-1/2} W^{1/2}$  is monomial
- output conductance  $g_o = \lambda I$  is monomial
- all capacitances are (approximately) posynomial in  $I, L, W$
- better (GP-compatible) models can be obtained by fitting data from accurate models or measurements


## Example: monomial $g_m$ model

- monomial model of  $g_m$  for I/O NMOS device in a  $0.13\mu\text{m}$  technology
- 11000 data points (from BSIM3) over ranges
  - $0.3\mu\text{m} \leq L \leq 3\mu\text{m}$ ,  $2\mu\text{m} \leq W \leq 20\mu\text{m}$
  - $0.7\text{V} \leq V_{\text{gs}} \leq 1.7\text{V}$ ,  $V_{\text{dsat}} \leq V_{\text{ds}} \leq 1.5V_{\text{gs}}$
- $V_{\text{ds}}$  appears in data set, but not in  $g_m$  model
- monomial fit (using simple log-regression, SI units):

$$g_m = 0.0278I^{0.4798}L^{-0.511}W^{0.5632}$$
 
## Example: monomial $g_m$ model

- fitting (relative) error cumulative distribution plot:




- for 90% of points, fit is better than 4%
 
# Single transistor common source amplifier

- variables:  $I$ ,  $L$ ,  $W$ ,  $R$
- saturation:  $V_{dsat} + IR \leq V_{dd}$
- gain  $G = g_m / (1/R + g_o)$
- power  $P = V_{dd}I$
- (unity gain) bandwidth  $B = g_m / C^L$
- design problem:

$$\begin{array}{ll} \text{minimize} & P \\ \text{subject to} & B \geq B^{\min}, \quad G \geq G^{\min} \\ & \text{saturation} \end{array}$$



## Common source amplifier design via GP

- rewrite as

$$\begin{array}{l} \text{minimize } P \\ \text{subject to } B^{-1} \leq 1/B^{\min}, \quad G^{-1} \leq 1/G^{\min} \\ V_{\text{dsat}} + IR \leq V_{\text{dd}} \end{array}$$

- . . . a **GP**, since  $P$  and  $B$  are monomials, and


$$G^{-1} = \frac{1/R + g_o}{g_m}$$

is posynomial

- this is a simple problem; don't need GP sledgehammer . . .



## Current mirror opamp

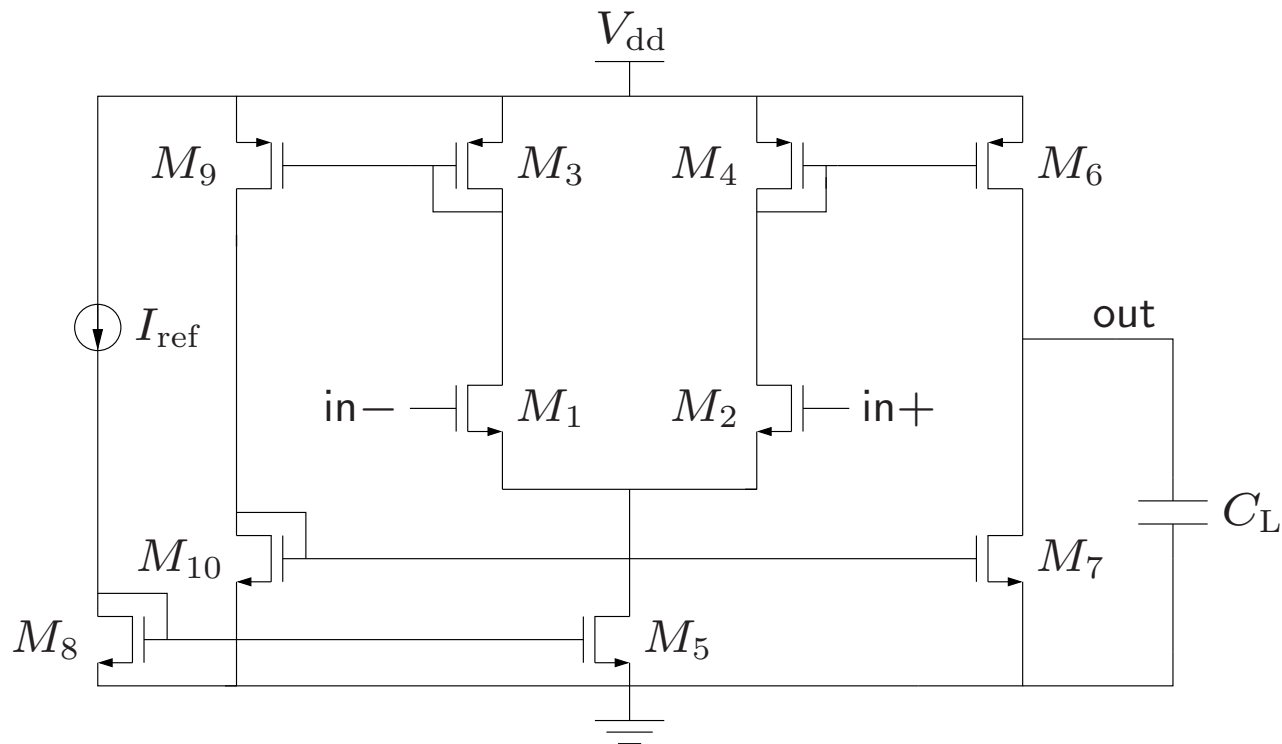

- $M_1, M_2$  and  $M_3, M_4$  matched pairs
- four current mirrors:  $M_8, M_5$ ;  $M_{10}, M_7$ ;  $M_9, M_3$ ;  $M_4, M_6$

## Design problem

minimize  $P$   
subject to  $B \geq B^{\min}$ ,  $G \geq G^{\min}$ ,  $A \leq A^{\max}$   
other constraints . . .

- objective & specifications:
  - $P$  is power dissipation
  - $B$  is unity gain bandwidth
  - $G$  is DC gain
  - $A$  is (active) area
- design variables:  $L_1, \dots, L_{10}, W_1, \dots, W_{10}$
- given:  $V_{\text{dd}}, C_L, I_{\text{ref}}$ , common-mode voltage  $V_{\text{cm}}$
- we'll formulate as GP

## Power, bandwidth, gain, & area

- power:  $P = V_{\text{dd}}(I_8 + I_5 + I_7 + I_{10})$  . . . posynomial
- bandwidth:  $B = g_{\text{m},2}g_{\text{m},6}/(g_{\text{m},4}C_{\text{L}})$  . . . monomial
- area:  $A = W_1L_1 + \dots + W_{10}L_{10}$  . . . posynomial
- gain:  $G = \frac{g_{\text{m},2}g_{\text{m},6}}{g_{\text{m},4}(g_{\text{o},6} + g_{\text{o},7})}$   
. . .  $G^{-1}$  is posynomial, so  $G \geq G^{\text{min}}$  can be written as  $G^{-1} \leq 1/G^{\text{min}}$

## Dimension, matching, and current constraints

- limits on device sizes:  $L_{\min} \leq L_i \leq L_{\max}$ ,  $W_{\min} \leq W_i$ ,  $i = 1, \dots, 10$
- differential symmetry constraints ( $M_1, M_2$  and  $M_3, M_4$  matched):

$$\begin{aligned} W_1 &= W_2, & L_1 &= L_2, & I_1 &= I_2, \\ W_3 &= W_4, & L_3 &= L_4, & I_3 &= I_4, \end{aligned}$$

- length & gate overdrive voltage matched for current mirror pairs:

$$\begin{aligned} L_5 &= L_8, & L_{10} &= L_7, & L_3 &= L_9, & L_4 &= L_6 \\ V_{\text{gov},5} &= V_{\text{gov},8}, & V_{\text{gov},10} &= V_{\text{gov},7}, & V_{\text{gov},3} &= V_{\text{gov},9}, & V_{\text{gov},4} &= V_{\text{gov},6} \end{aligned}$$

- current relations:

$$I_1 = I_3 = I_5/2, \quad I_8 = I_{\text{ref}}, \quad I_6 = I_7, \quad I_9 = I_{10}$$

## Saturation constraints

- diode connected devices ( $M_3, M_4, M_8, M_{10}$ ) automatically in saturation
- others must have  $V_{ds} \geq V_{dsat}$ :
  - $M_7$ :  $V_{dsat,7} \leq V_{cm}$
  - $M_6$ :  $V_{dsat,6} + V_{cm} \leq V_{dd}$
  - $M_9$ :  $V_{dsat,9} + V_{gs,10} \leq V_{dd}$
  - $M_5$ :  $V_{ds,5} + V_{gs,1} \leq V_{cm}$
  - $M_1$  &  $M_2$ :  $V_{cm} + V_{gs,3} \leq V_{dd} + V_{th}$
- . . . all are posynomial inequalities

## Node capacitances and non-dominant poles

- capacitances at nodes are posynomials, *e.g.*,

$$C^{\text{out}} = C_{\text{gd},6} + C_{\text{db},6} + C_{\text{gd},7} + C_{\text{db},7} + C_L$$

- non-dominant time constants are posynomials:

$$\tau_1 = \frac{C_{\text{d}1}}{g_{\text{m},3}}, \quad \tau_2 = \frac{C_{\text{d}2}}{g_{\text{m},4}}, \quad \tau_9 = \frac{C_{\text{d}9}}{g_{\text{m},10}}$$


( $C_{\text{d}1}, C_{\text{d}2}, C_{\text{d}9}$  are node capacitances at drains of  $M_1, M_2, M_9$ )

- to limit effect of non-dominant poles, make sum smaller than dominant time constant:

$$\tau_1 + \tau_2 + \tau_9 \leq \tau_{\text{dom}} = C_L/g_m$$


. . . a posynomial constraint

# Power versus bandwidth trade-off

 
 
## Joint electrical/physical design


- each device has a (physical) cell width  $w$  and height  $h$  for floor planning
- devices are folded into multiple fingers
- (approximate) posynomial or monomial relations link electrical variables ( $I$ ,  $L$ ,  $W$ ) and physical variables ( $w$ ,  $h$ ), e.g.,
  - cell area is at least  $4\times$  active area:  $wh \geq 4WL$
  - cell aspect ratio limited to 5:1:  $1/5 \leq w/h \leq 5$




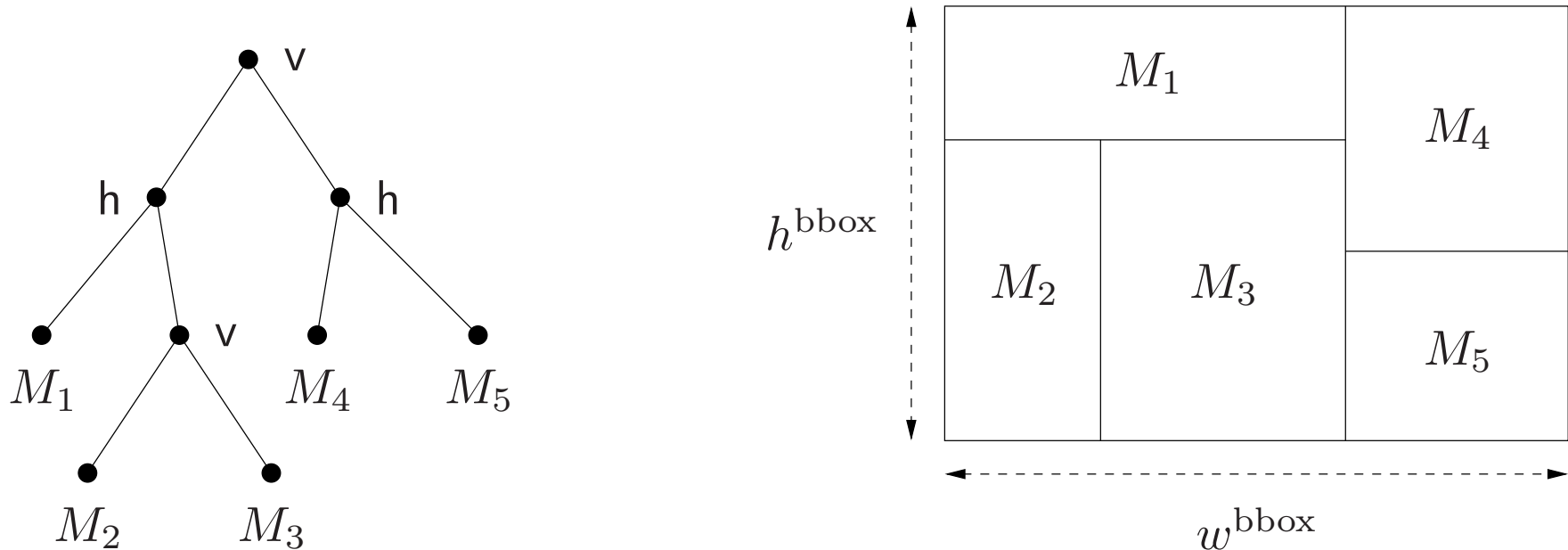
## Slicing tree layout scheme

- vertical and horizontal slices fix relative placement of device cells
- leaves are device cells; root is bounding box



## Slicing tree constraints

- introduce width, height for each node in slicing tree
- for each vertical slice with parent  $a$  and children  $b, c$  add constraints

$$w_a = w_b + w_c, \quad h_a = \max\{h_b, h_c\}$$

- for each horizontal slice with parent  $a$  and children  $b, c$  add constraints

$$w_a = \max\{w_b, w_c\}, \quad h_a = h_b + h_c$$


- shows width and height of bounding box and each node is generalized posynomial of device cell widths, heights
- resulting GP formulation is very sparse

# Joint electrical/physical design via GP

- form **one** GP that includes
  - electrical variables, constraints ( $I_i, L_i, W_i, g_{m,i} \dots$ )
  - physical variables, constraints ( $w_i, h_i, w^{\text{bbox}}, h^{\text{bbox}}, \dots$ )
  - coupling constraints ( $w_i h_i \geq 4W_i L_i, \dots$ )
- solve it all together
- extensions: can add
  - parasitic estimates
  - more accurate expressions for device cell dimensions
  - channels for routing

# Optimal filter implementation

simple Gm-C two-pole lowpass filter

 

transfer function is

$$H(s) = \frac{1}{1 + t_1s + t_1t_2s^2}, \quad t_1 = C_1/g_1, \quad t_2 = C_2/g_2$$

$g_i$  is amplifier transconductance

## Noise analysis

- $N_i$  is input referred (white) amplifier input-referred voltage density
- spectral density of output noise is

$$N(\omega)^2 = \frac{N_1^2 + \omega^2 N_2^2}{(1 - t_1 t_2 \omega^2)^2 + t_1^2 \omega^2}$$

- root-mean-square output noise voltage is

$$M = \left( \int_0^\infty N(\omega)^2 d\omega \right)^{1/2} = (\alpha N_1^2 + \beta N_2^2)^{1/2}$$

## Amplifier and capacitor implementation models

- each amplifier has **private variables**  $u$  (*e.g.*, device lengths & widths) and constraints
- transconductance  $g$  is monomial in  $u$ ; area  $A^{\text{amp}}$ , power  $P$ , input-referred noise density  $N$  are posynomial in  $u$
- each capacitor has private variables  $v$  (*e.g.*, physical dimensions) and constraints
- capacitance  $C$  is monomial in  $v$ ; area  $A^{\text{cap}}$  is posynomial
- design variables are  $u_1, u_2, v_1, v_2$

## Optimal filter implementation problem

- filter is Butterworth with frequency  $\omega_c$ :

$$t_1 = \sqrt{2}/\omega_c, \quad t_2 = (1/\sqrt{2})/\omega_c$$

- minimize total power of implementation, subject to area, output noise limits:

$$\text{minimize } P(u_1) + P(u_2)$$

$$\text{subject to } t_1 = \sqrt{2}/\omega_c, \quad t_2 = (1/\sqrt{2})/\omega_c$$

$$A^{\text{amp}}(u_1) + A^{\text{amp}}(u_2) + A^{\text{cap}}(v_1) + A^{\text{cap}}(v_2) \leq A^{\text{max}}$$

$$M = (\omega_c/4\sqrt{2})(N_1^2 + 2N_2^2)^{1/2} \leq M^{\text{max}}$$

- a **GQP** in the variables  $u_1, u_2, v_1, v_2$

## Example

- Butterworth filter with  $\omega_c = 10^8 \text{ rad/s}$
- private variables in amplifiers: (equivalent)  $L, W$
- amplifier model:


$$A^{\text{amp}} = WL, \quad P = 2.5 \cdot 10^{-4} W/L,$$
$$g = 4 \cdot 10^{-5} W/L, \quad N = \sqrt{7.5 \cdot 10^{-16} L/W}$$

(based on simple model with  $V_{\text{dd}} = 2.5, V_{\text{gov}} = 0.2$ )


- private variable in capacitors is area  $A^{\text{cap}}$ ;  $C = 10^{-4} A^{\text{cap}}$
- $A^{\text{max}} = 4 \cdot 10^{-6}$



## Power versus noise trade-off

 
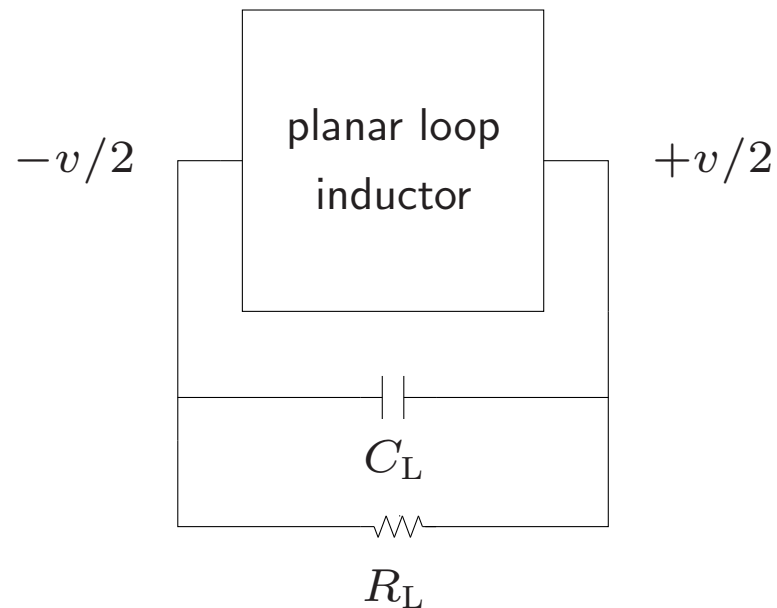
## Spiral inductor/differential resonator optimization




- loop inductor connected to (given)  $R_L$  and  $C_L$
- differential (floating) mode operation
- inductor designed to resonate at operating frequency  $f$

## Design problem: differential resonator

$$\begin{aligned} & \text{maximize} && R_T \\ & \text{subject to} && Q_T \geq Q_T^{\min}, \quad A \leq A^{\max} \\ & && \text{other constraints} \dots \end{aligned}$$


- objective & specifications:
  - $R_T$  is tank impedance (which is real at operating frequency  $f$ )
  - $Q_T$  is tank quality factor
  - $A$  is area of loop inductor
- design variables: dimensions of loop inductor
- load resistance  $R_L$ , load capacitance  $C_L$ , frequency  $f$  given
- we'll formulate as GP

## Loop inductor

 

- (centerline) diameter  $D$
- width  $W$
- outer diameter is  $D + W$ ; area is  $A = (D + W)^2$

## Lumped model for loop inductor

 

- lumped model for operation in differential mode
- impact of substrate capacitance, loss included in  $R$  and  $C$

## Example

- frequency range  $2\text{GHz} \leq f \leq 6\text{GHz}$
- metal layer thickness  $2\mu\text{m}$ , resistivity  $5 \cdot 10^{-8}\Omega\text{m}$
- metal-substrate capacitance density  $5 \cdot 10^{-6}\text{Fm}^2$
- width, diameter constraints:

$$150\mu\text{m} \leq D \leq 600\mu\text{m}, \quad 4\mu\text{m} \leq W \leq 30\mu\text{m}, \quad 10 \leq D/W \leq 100$$

## GP models for $L$ , $R$ and $C$

- can get exact values via EM simulation
- inductance (monomial)

$$L = 2.1 \cdot 10^{-6} D^{1.28} W^{-0.25} f^{-0.01}$$


- resistance (posynomial)

$$R = 0.1 DW^{-1} + 3 \cdot 10^{-6} DW^{-0.84} f^{0.5} + 5 \cdot 10^{-9} DW^{-0.76} f^{0.75} + 0.02 DW f$$

- capacitance (posynomial):

$$C = 5 \cdot 10^{-6} DW + 1 \cdot 10^{-11} D$$


## Resonance constraint

 

- resonance condition:  $4\pi^2 f^2 LC_T = 1$  ( $C_T = C + C_L$ )
- to handle in GP:
  - impose posynomial constraint  $C + C_L \leq C_T$
  - add extra capacitance (after design)  $C_{\text{extra}} = C_T - C - C_L$  if needed




## Tank conductance and quality factor

 


- tank conductance:  $G_T = \frac{1}{R_T} = \frac{R}{4\pi^2 f^2 L^2} + \frac{1}{R_L}$  . . . posynomial
- inverse of tank quality factor:  $\frac{1}{Q_T} = \frac{R}{2\pi f L} + \frac{2\pi f L}{R_L}$  . . . posynomial
 
## Resonance impedance versus area trade-off



# LC oscillator

 


- loop inductor
- varactors for fine tuning
- binary weighted switching capacitors for coarse tuning
- cross coupled NMOS transistors
- tail current source

## LC oscillator design problem

minimize  $P$   
subject to  $N \leq N^{\max}$ ,  $A \leq A^{\max}$ ,  $l \geq l^{\min}$   
other constraints . . .

- objective & specifications:
  - $P$  is power consumption
  - $N$  is phase noise
  - $A$  is area of loop inductor
  - $l$  is loop gain
- given: load capacitance  $C_L$ , center frequency  $f$ , normalized tuning range  $T$
- we'll formulate as GP

## Design variables

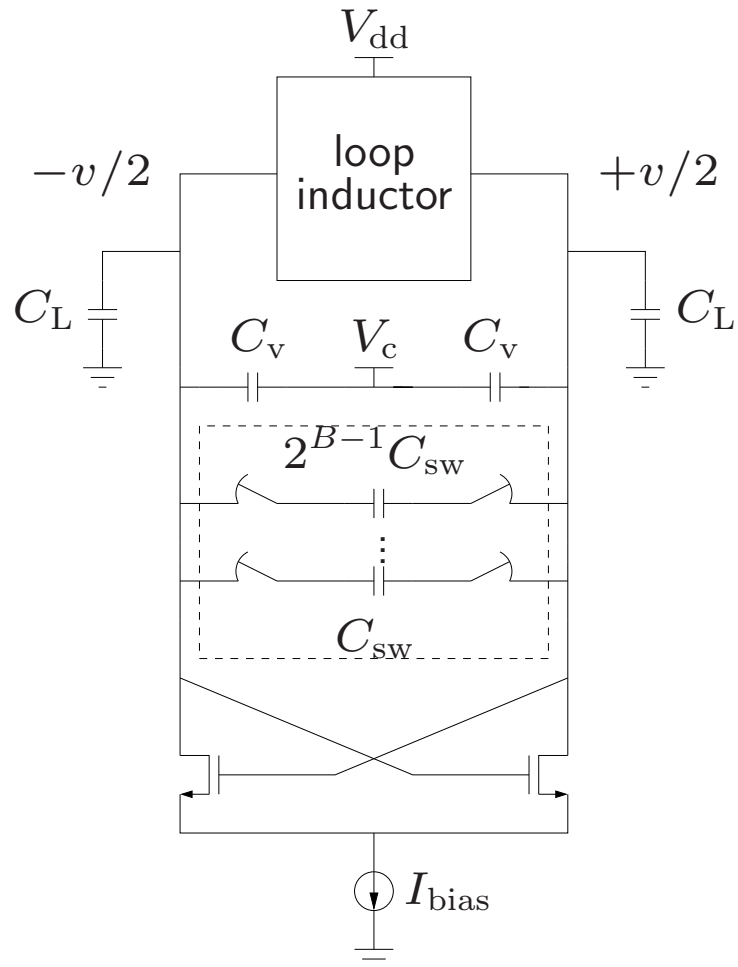

- loop inductor dimensions  $D, W$
- size of varactor  $V_c$
- size of switching capacitors  $C_{sw}$
- width, length of transistors  
 $W_{nmos}, L_{nmos}$
- bias current  $I_{bias}$

# Current source, switched capacitor, and varactor models

- $I_{\text{bias}}$  is bias current, with minimum operating voltage  $V_{\text{bias}}$
- binary weighted capacitors
  - $B$  is number of bits for switching capacitors
  - $C_{\text{sw}}$  is LSB switching capacitance;  $2^{B-1}C_{\text{sw}}$  is MSB switching capacitance
- varactor
  - $C_{\text{v}}$  is minimum varactor capacitance;  $K_{\text{v}}C_{\text{v}}$  is maximum ( $K_{\text{v}}$  is process constant)
  - varactor range covers 2 LSB:  $2C_{\text{sw}} \leq 0.5(K_{\text{v}} - 1)C_{\text{v}}$

## Tank capacitance

- tank capacitance is sum of  $C_{\text{fix}}$  and  $C_{\text{tune}}$
- fixed capacitance is sum of loop, load and transistor capacitances:

$$C_{\text{fix}} = C + 0.5 (C_L + C_{\text{gs}} + 4C_{\text{gd}} + C_{\text{db}})$$

- tunable capacitance is sum of switching and varactor capacitances:
  - $C_{\text{tune}}$  for maximum frequency:  $C_{\text{tune}} = 0.5C_v$
  - $C_{\text{tune}}$  for minimum frequency:  $C_{\text{tune}} = 2^B C_{\text{sw}} + 0.5K_v C_v$

## Resonance frequency & tuning

- capacitance constraint at maximum frequency:  $C_{\text{fix}} + 0.5C_{\text{v}} \leq C_{\text{f,max}}$
- maximum frequency:  $(2\pi f(1 + T))^2 LC_{\text{f,max}} = 1$
- capacitance at center frequency:  $(2\pi f)^2 LC_{\text{f,c}} = 1$
- tuning range constraint:

$$\frac{4T}{(1 - T^2)^2} C_{\text{f,c}} \leq C_{\text{sw}} (2^B + 2)$$



## Power & area

- power:  $P = V_{\text{dd}}I_{\text{bias}}$
- area:  $A = (D + W)^2 + 2W_{\text{nmos}}L_{\text{nmos}}$   
(can add area of switched capacitors, varactor)

## Tank conductance & voltage swing

- tank conductance is posynomial:  $G_T = \frac{R}{4\pi^2 f^2 L^2} + 0.5g_o$
- differential voltage amplitude:  $V_{osc} + 2V_{bias} \leq 2V_{dd}$ ,  $V_{osc}G_T \leq I_{bias}$

## Phase noise

- thermal current noise power density of loop:  $\overline{i_{n,L}^2} = \frac{4kTR}{4\pi^2 f^2 L^2}$
- thermal current noise power density of transistor:  $\overline{i_{nmos}^2} = 4kT\gamma g_m$
- phase noise in the  $1/f^2$  region:

$$N = \frac{1}{16\pi^2 f_{\text{off}}^2 C_T^2 V_{\text{osc}}^2} \left( \overline{i_{n,L}^2} + 0.5 \overline{i_{nmos}^2} \right)$$

- . . . can add other noise terms

## Loop gain and start-up

- inverse of loop gain is posynomial:  $1/l = (g_o + 2G)/g_m$
- minimum loop gain to ensure start-up:  $l \geq l^{\min}$
- bias condition for quiescent operating point:  $V_{\text{bias}} + V_{\text{gs}} + \frac{I_{\text{bias}}R}{4} \leq V_{\text{dd}}$
- NMOS device models:


$$g_m = 4.5 \cdot 10^{-3} W_{\text{nmos}}^{0.6} L_{\text{nmos}}^{-0.6} I_{\text{bias}}^{0.4}$$

$$g_o = 2.6 \cdot 10^{-10} W_{\text{nmos}}^{0.4} L_{\text{nmos}}^{-1.4} I_{\text{bias}}^{0.6}$$


$$V_{\text{gs}} = 0.34 + 1 \cdot 10^{-8} L_{\text{nmos}}^{-1} + 5 \cdot 10^2 W_{\text{nmos}}^{-0.7} L_{\text{nmos}}^{0.7} I_{\text{bias}}^{0.7}$$
 
## LC oscillator example

- center frequency:  $f = 5\text{GHz}$
- tuning range:  $T = \pm 10\%$
- varactor tuning ratio:  $K_v = 3$
- $B = 3$ bits switching capacitor
- minimum loop gain:  $l^{\min} = 2$
- load capacitance:  $C_L = 200\text{fF}$
- supply voltage:  $V_{\text{dd}} = 1.2\text{V}$
- offset frequency for phase noise:  $f_{\text{off}} = 600\text{kHz}$



## Power versus phase noise trade-off

 

# Monomial and Posynomial Fitting

## A basic property of posynomials

- if  $f$  is a monomial, then  $\log f(e^y)$  is **affine** (linear plus constant)
- if  $f$  is a posynomial, then  $\log f(e^y)$  is **convex**
- roughly speaking, a posynomial is convex when plotted on log-log plot
- midpoint rule for posynomial  $f$ :
  - let  $z$  be elementwise geometric mean of  $x, y$ , *i.e.*,  $z_i = \sqrt{x_i y_i}$
  - then  $f(z) \leq \sqrt{f(x)f(y)}$
- a converse: if  $\log \phi(e^y)$  is convex, then  $\phi$  can be approximated as well as you like by a posynomial



## Convexity in circuit design context


- consider circuit with design variables  $W_1, \dots, W_n$  (say) & performance measure  $\phi(W_1, \dots, W_n)$  (e.g., power, delay, area)
- two designs:  $W_i^{(a)}$  &  $W_i^{(b)}$ , with performance  $\phi^{(a)}$  &  $\phi^{(b)}$
- form **geometric mean** compromise design with  $W_i^{(c)} = \sqrt{W_i^{(a)}W_i^{(b)}}$ , performance  $\phi^{(c)}$
- if  $\phi$  is generalized posynomial, then we have  $\phi^{(c)} \leq \sqrt{\phi^{(a)}\phi^{(b)}}$
- this is **not obvious**

# Monomial/posynomial approximation: Theory

when can a function  $f$  be approximated by a monomial or generalized posynomial?

- form function  $F(y) = \log f(e^y)$
- $f$  can be approximated by a monomial if and only if  $F$  is nearly affine (linear plus constant)
- $f$  can be approximated by a generalized posynomial if and only if  $F$  is nearly convex

## Examples

 

- $\tanh(x)$  can be reasonably well fit by a monomial
- $0.5/(1.5 - x)$  can be fit by a generalized posynomial
- $(2/\sqrt{\pi}) \int_x^\infty e^{-t^2} dt$  cannot be fit very well by a generalized posynomial

## What problems can be approximated by GGPs?

$$\begin{array}{ll} \text{minimize} & f_0(x) \\ \text{subject to} & f_i(x) \leq 1, \quad i = 1, \dots, m \\ & g_i(x) = 1, \quad i = 1, \dots, p \end{array}$$

- transformed objective and inequality constraint functions  $F_i(y) = \log f_i(e^y)$  must be nearly convex
- transformed equality constraint functions  $G_i(y) = \log G_i(e^y)$  must be nearly affine

## Monomial fitting via log-regression

find coefficient  $c > 0$  and exponents  $a_1, \dots, a_n$  of monomial  $f$  so that

$$f(x^{(i)}) \approx f^{(i)}, \quad i = 1, \dots, N$$

- rewrite as

$$\begin{aligned} \log f(x^{(i)}) &= \log c + a_1 \log x_1^{(i)} + \dots + a_n \log x_n^{(i)} \\ &\approx \log f^{(i)}, \quad i = 1, \dots, N \end{aligned}$$

- use least-squares (regression) to find  $\log c, a_1, \dots, a_n$  that minimize

$$\sum_{i=1}^N \left( \log c + a_1 \log x_1^{(i)} + \dots + a_n \log x_n^{(i)} - \log f^{(i)} \right)^2$$

## Posynomial fitting via Gauss-Newton

find coefficients and exponents of posynomial  $f$  so that

$$f(x^{(i)}) \approx f^{(i)}, \quad i = 1, \dots, N$$

- minimize sum of squared fractional errors


$$\sum_{i=1}^N \left( \frac{f^{(i)} - f(x^{(i)})}{f^{(i)}} \right)^2$$

can be (locally) solved by Gauss-Newton method

- needs starting guess for coefficients, exponents
 
## Posynomial fitting example

- 1000 data points from  $f(x) = e^{(\log x_1)^2 + (\log x_2)^2}$  over  $0.1 \leq x_i \leq 1$
- cumulative error distribution for 3-, 5-, and 7-term posynomial fits



## A simple max-monomial fitting method

fit **max-monomial**

$$f(x) = \max_{k=1,\dots,K} f_k(x)$$

( $f_1, \dots, f_k$  monomials) to data  $x^{(i)}, f^{(i)}, i = 1, \dots, N$

simple algorithm:

**repeat**


**for**  $k = 1, \dots, K$

1. find all data points  $x^{(j)}$  for which  $f_k(x^{(j)}) = f(x^{(j)})$   
(*i.e.*, data points at which  $f_k$  is the largest of the monomials)
2. update  $f_k$  by carrying out monomial fit to these data


 
## Max-monomial fitting example

- same 1000 data points as previous example
- cumulative error distribution for 3-, 5-, and 7-term max-monomial fits



# Conclusions

# Conclusions

(generalized) geometric programming

- comes up in a variety of circuit sizing contexts
- can be used to formulate a variety of problems
- admits fast, reliable solution of large-scale problems
- is good at concurrently balancing lots of coupled constraints and objectives
- is useful even when problem has discrete constraints

# Approach

- most problems don't come naturally in GP form; be prepared to reformulate and/or approximate
- GP modeling is not a “try my software” method; it requires thinking
- our approach:
  - start with simple analytical models (RC, square-law, Pelgrom, . . . ) to verify GP might apply
  - then fit GP-compatible models to simulation or measured data
  - for highest accuracy, revert to local method for final polishing

- looking for keys under street light  
(not where keys were lost, but lighting is good)
  
- forcing problems into GP-compatible form  
(problems aren't GPs, but solving is good)

## References

- *A tutorial on geometric programming*
- *Digital circuit sizing via geometric programming*
- *Analog circuit design via geometric programming*
- *Convex optimization*, Cambridge Univ. Press 2004

(these include hundreds of references)

available at [www.stanford.edu/~boyd/research.html](http://www.stanford.edu/~boyd/research.html)

# Software

- MOSEK: [www.mosek.com](http://www.mosek.com)
- COPL-GP: (Yinyu Ye, in process of being re-worked):  
[www.stanford.edu/~yyye/Col.html](http://www.stanford.edu/~yyye/Col.html)
- GPGLP: <ftp://ftp.pitt.edu/dept/ie/GP/>
- YALMIP: [control.ee.ethz.ch/~joloef/yalmip.msql](http://control.ee.ethz.ch/~joloef/yalmip.msql)
- a simple matlab GP solver `gp.m` at Boyd's EE364 site