

CMOS Op-amp Design and Optimization via Geometric Programming

Mar Hershenson, **Stephen Boyd**, Thomas Lee

Electrical Engineering Department
Stanford University

UCSB 10/24/97

CMOS analog amplifier design

problem: choose transistor dimensions, bias currents, component values

- critical part of mixed-mode (digital-analog) ICs
- for typical mixed-mode IC,
 - 1:10 analog:digital area
 - 10:1 analog:digital design time

this talk: a **new method** for CMOS op-amp design, based on **geometric programming**

- **globally optimal** and **extremely fast**
- handles wide variety of practical constraints & specs

Outline

- Geometric programming
- Two-stage op-amp
- MOS models
- Constraints & specs
- Design examples & trade-off curves
- Extensions
- Conclusions

Monomial & posynomial functions

$x = (x_1, \dots, x_n)$: vector of positive variables

function g of form

$$g(x) = x_1^{\alpha_1} x_2^{\alpha_2} \dots x_n^{\alpha_n},$$

with $\alpha_i \in \mathbf{R}$, is called **monomial**

function f of form

$$f(x) = \sum_{k=1}^t c_k x_1^{\alpha_{1k}} x_2^{\alpha_{2k}} \dots x_n^{\alpha_{nk}},$$

with $c_k \geq 0$, $\alpha_{ik} \in \mathbf{R}$, is called **posynomial**

- posynomials closed under sums, products, nonnegative scaling
- monomials closed under products, division, nonnegative scaling
- if $1/f$ is posynomial we say f is **inverse posynomial**

examples:

- $0.1x_1x_3^{-0.5} + x_2^{1.5}x_3^{0.7}$ is posynomial
- $1/(1 + x_1x_2^{1.3})$ is inverse-posynomial
- $2x_3\sqrt{x_1/x_2}$ is monomial (hence also posy. & inv-posy.)

Geometric programming

a special form of optimization problem:

$$\begin{aligned} & \text{minimize} && f_0(x) \\ & \text{subject to} && f_i(x) \leq 1, \quad i = 1, \dots, m \\ & && g_i(x) = 1, \quad i = 1, \dots, p \\ & && x_i > 0, \quad i = 1, \dots, n \end{aligned}$$

where f_i are posynomial and g_i are monomial

more generally with geometric programming we can

- **minimize** any posynomial or monomial function, or
- **maximize** any inverse-posynomial or monomial function


subject to any combination of

- **upper bounds** on posynomial or monomial functions
- **lower bounds** on inverse-posynomial or monomial functions
- **equality constraints** between monomial functions

Geometric programming: history & methods


- used in engineering since 1967 (Duffin, Peterson, Zener)
 - used for digital circuit transistor sizing with Elmore delay since 1980 (Fishburn & Dunlap's TILOS)
- new (interior-point) methods for GP (*e.g.*, Kortanek et al)
- are **extremely fast**
 - handle medium and large-scale problems (100s vbles, 1000s constraints easily solved on PC in minutes)
 - either find **global optimal** solution, or provide **proof of infeasibility**

Two-stage op-amp

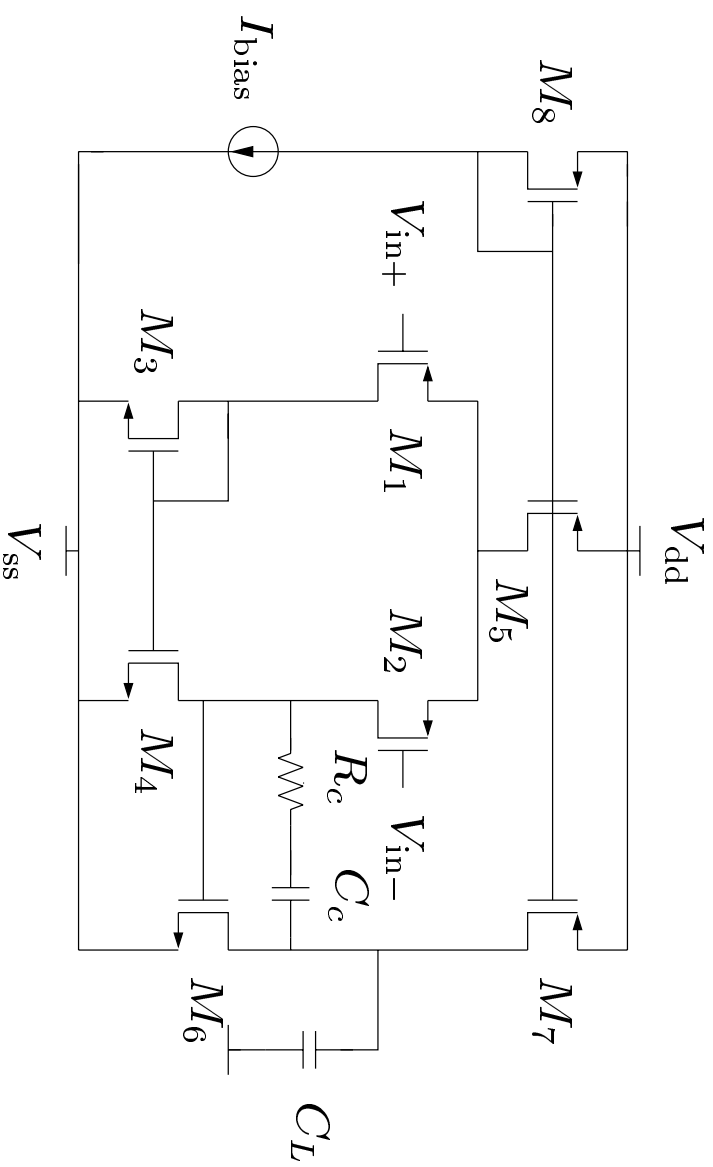

- common op-amp architecture
- **19 design variables:** $W_1, \dots, W_8, L_1, \dots, L_8, R_c, C_c, I_{bias}$

Large signal MOS model

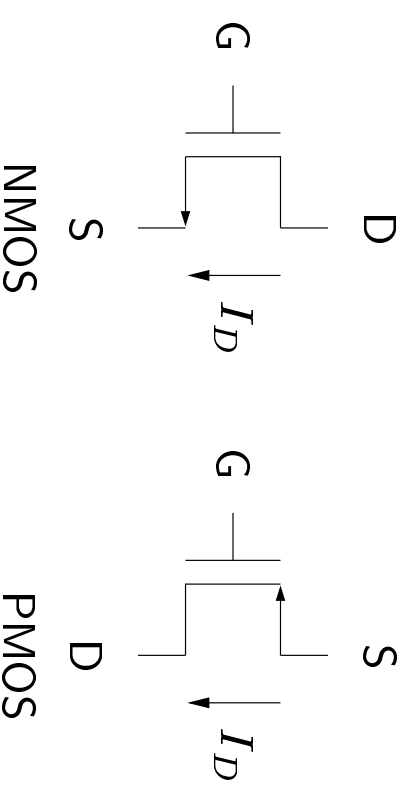


NIMOS saturation condition: $V_{DS} \geq V_{GS} \Leftrightarrow V_{TN}$

square-law model $I_D = k_1 (W/L)(V_{GS} \Leftrightarrow V_{TN})^2$

similar condition & model for PMOS

(more accurate model possible, *e.g.*, for short channel)

Small signal dynamic MOS model

 

transconductance and output conductance,

$$g_m = k_2 \sqrt{I_D W/L}, \quad g_o = k_3 I_D$$

are **monomial** in W , L , I_D

capacitances are all (approximately) posynomial in W , L , I_D

Dimension constraints

limits on device sizes:

$$L_{\min} \leq L_i \leq L_{\max}, \quad W_{\min} \leq W_i \leq W_{\max}$$

(express as $L_i/L_{\max} \leq 1$, etc.)

symmetry constraints: $W_1 = W_2$, $L_1 = L_2$, $W_3 = W_4$, $L_3 = L_4$

bias transistor matching: $L_5 = L_7 = L_8$

to reduce systematic input offset voltage:

$$\frac{W_3/L_3}{W_6/L_6} = \frac{W_4/L_4}{W_6/L_6} = \frac{W_5/L_5}{2W_7/L_7}$$

area = $\alpha_1 C_c + \alpha_2 \sum_i W_i L_i$ is posynomial, hence can impose upper limit

Bias constraints

each transistor must remain in saturation over specified

- common-mode input range [$V_{\text{cm},\text{min}}$, $V_{\text{cm},\text{max}}$]
- output voltage swing [$V_{\text{out},\text{min}}$, $V_{\text{out},\text{max}}$]

leads to four **posynomial inequalities**

e.g., for M_5 we get

$$k_4 \sqrt{\frac{I_1 L_1}{W_1}} + k_5 \sqrt{\frac{I_5 L_5}{W_1}} \leq V_{\text{dd}} \Leftrightarrow V_{\text{cm},\text{max}} + V_{\text{TP}}$$

(every drain current is monomial in the design variables)

Quiescent power & slew rate specs

quiescent power is posynomial:

$$P = (V_{\text{dd}} \Leftrightarrow V_{\text{ss}}) (I_{\text{bias}} + I_5 + I_7)$$

hence can impose upper limit on power (or minimize it)

slew rate is

$$\min \left\{ \frac{2I_1}{C_c}, \frac{I_7}{C_c + C_L} \right\}$$

min slew rate spec can be expressed as posynomial inequalities

$$\frac{C_c \text{SR}_{\min}}{2I_1} \leq 1, \quad \frac{(C_c + C_L) \text{SR}_{\min}}{I_7} \leq 1$$

Transfer function

with standard value $R_c = 1/g_{m6}$, TF is accurately given by

$$H(s) = \frac{A_v}{(1 + s/p_1)(1 + s/p_2)(1 + s/p_3)(1 + s/p_4)}$$

- open-loop gain is **monomial**: $A_v = k_6 \sqrt{W_2 W_6 / L_2 L_6 I_1 I_7}$
- dominant pole p_1 is **monomial**: $p_1 = g_{m1} / A_v C_c$
- parasitic poles p_2, p_3, p_4 are **inverse posynomial**

hence can fix the open-loop gain and dominant pole, and lower bound the parasitic poles

3 dB bandwidth and unity gain crossover specs

- **bandwidth constraints:** $|H(j\omega)| \geq a$ for $\omega \leq \Omega$

$$\Leftrightarrow |H(j\Omega)|^2 = \frac{A_v^2}{(1 + \Omega^2/p_1^2)(1 + \Omega^2/p_2^2)(1 + \Omega^2/p_3^2)(1 + \Omega^2/p_4^2)} \geq a^2$$

$$\Leftrightarrow (a^2/A_v^2)(1 + \Omega^2/p_1^2)(1 + \Omega^2/p_2^2)(1 + \Omega^2/p_3^2)(1 + \Omega^2/p_4^2) \leq 1$$

- . . . a posynomial inequality (since p_i are inv.-pos.)
- **unity gain crossover** is (very accurately) monomial: $\omega_c = g_{m1}/C_c$
- hence can fix (or upper or lower bound) crossover frequency

Phase margin specs

min phase margin spec is:

$$\Leftrightarrow \angle H(j\omega_c) = \sum_{i=1}^4 \arctan(\omega_c/p_i) \leq \pi \Leftrightarrow \text{PM}_{\min}$$

extremely good approximation:

$$\sum_{i=2}^4 \omega_c/p_i \leq \pi/2 \Leftrightarrow \text{PM}_{\min}$$

(since p_1 contributes 90° , and $\arctan(x) \approx x$ for $x \leq 50^\circ$)

... a **posynomial inequality** since parasitic poles are **inverse posynomial**

Other specs

- min common-mode rejection ratio
- min (pos. & neg.) power supply rejection ratios
- max spot noise at any frequency
- max total RMS noise over any frequency band
- min gate overdrive

can all be handled by geometric programming

Summary

using **geometric programming** we can **globally optimize** a design involving all the specs described above:

- dimension constraints, area
- bias constraints, power, slew rate
- bandwidth, crossover frequencies, phase margin
- CMRR, nPSRR, pPSRR
- spot & total noise

typical problem:

- approx 20 vbles, 10 equality & 20 inequality constraints
- solution time \approx 1 sec (inefficient Matlab implementation!)

(Globally) optimal trade-off curves

- fix all specs except one (*e.g.*, power)
- optimize objective (*e.g.*, maximize crossover frequency) for different values of spec
- yields **globally optimal** trade-off curve between objective and spec (with others fixed)


Default specs

our examples will maximize crossover BW with default specs


- $V_{dd} = 5V$, $V_{ss} = 0V$, $1.2\mu\text{m}$ process
- $L_i \geq 0.8\mu\text{m}$, $W_i \geq 2\mu\text{m}$, area $\leq 10000\mu\text{m}^2$
- CM input fixed at mid-supply; output range is 10%–90% of supply
- power $\leq 5\text{mW}$
- open-loop gain $\geq 80\text{dB}$, PM $\geq 60^\circ$
- slew rate $\geq 10V/\mu\text{sec}$
- CMRR $\geq 60\text{dB}$
- input-referred spot noise (1kHz) $\leq 300\text{nV}/\sqrt{\text{Hz}}$

(we'll vary one or more to get trade-off curves)


Maximum BW versus power & supply voltage

 


Minimum noise versus power & BW

 

 Maximum BW versus power & load capacitance



Maximum BW versus area & power

 

Extensions

- can solve large coupled problems
(*e.g.*, total area, power for IC with 100 op-amps)
- can do **robust design** that works with several process conditions
- get sensitivities for free
- method extends to wide variety of amplifier architectures, BJTs, etc.
- can use far better (monomial) MOS models, *e.g.*, for short-channel designs

Conclusions

- using **geometric programming** we can **globally** and **efficiently** solve CMOS op-amp design problems
 - allows designer to spend more time **designing**, *i.e.*, exploring trade-offs between competing objectives (power, area, bandwidth,)
 - yields **completely automated** synthesis of CMOS op-amps **directly from specifications**
 - huge reduction in analog design time
- (cf. methods based on simulated annealing, expert systems, general nonlinear programming,)